

CS3350B Computer Organization

Chapter 2: Synchronous Circuits

Part 2: Stateless Circuits

Iqra Batool

Department of Computer Science
University of Western Ontario, Canada

Wednesday January 31, 2024

Outline

- 1 Combinational Circuits
- 2 Adders and Subtractors
- 3 MUX and DEMUX
- 4 Arithmetic Logic Units

Stateless Circuits are Combinational Circuits

- **Stateless** \Rightarrow No memory.
- **Combinational** \Rightarrow Output is a combination of the inputs alone.

Combinational circuits are formed from a combination of logic gates and other combinational circuits.

- ↳ Modular Design,
- ↳ Reuse,
- ↳ Simple to add new components.

Sometimes, these are called **functional blocks**, they implement *functions*.


Increasing Arity

Arity: the number of inputs to a gate, function, etc.

How can we build an n -way add from simple 2-input and gates?

↳ Simply chain together $n - 1$ 2-way gates.

Example: 5-way AND

 


Works for AND, OR, XOR. *Doesn't* work for NAND, NOR.

Block Diagrams

A **block diagram** or **schematic diagram** can be used to express the high-level specification of a circuit.

 
- How many inputs, how many bits for each input?
- How many outputs, how many bits for each output?
- What does the circuit do? Formula or truth table.



$$F \equiv \overline{abc} + abc$$

a	b	c	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

From Blocks to Gates (1/2)

 

- 1 Generate truth table.
- 2 Get canonical form:

a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$F \equiv \bar{a}bc + a\bar{b}c + ab\bar{c} + abc$$

- 3 Simplify if possible:


$$\bar{a}bc + a\bar{b}c + ab\bar{c} + abc$$

$$\equiv \bar{a}bc + a\bar{b}c + ab\bar{c} + abc + abc + abc$$

$$\equiv \bar{a}bc + abc + a\bar{b}c + abc + ab\bar{c} + abc$$

$$\equiv bc + ac + ab$$

From Blocks to Gates (2/2)

 


<i>a</i>	<i>b</i>	<i>c</i>	<i>F</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

3 Simplify if possible:

$$F \equiv bc + ac + ab$$

 4 Draw your circuit from simplified formula.




This is called a *majority* circuit. Output is true iff majority of inputs are true.

Outline

- 1 Combinational Circuits
- 2 Adders and Subtractors
- 3 MUX and DEMUX
- 4 Arithmetic Logic Units

1 Bit Adder

 
Adder interprets bits as a binary number and does addition.



a	b	s	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s = \text{add}(a, b)$$



c = carry (overflow) bit

 

1 Bit Full Adder

Full Adder does addition of 3 inputs: a , b , and carry_{in} .

↳ Previous adder was a *half* adder.

  


$$s = (a \text{ XOR } b) \text{ XOR } c_{in}$$

$$c = ab + (\text{XOR}(a, b) \cdot c_{in})$$

1 Bit Full Adder using Half Adders

A full adder can be built from half adders.

 
↳ Modular design, reuse, simplified view.



n-Bit Full Adder

n-bit adder: Add n bits with carry.

 - ↳ Just like long addition done by hand.
- ↳ Combine n full adders, adding bit by bit, carrying the carry from lowest-ordered bit to highest-ordered bit.
- ↳ Final carry bit is c_n .



Addition Overflow (1/2)

Overflow occurs when arithmetic results in a number strictly larger than can fit in the predetermined number of bits.

- For *unsigned* integers, overflow is detected by c_n being 1.
- For *signed* (i.e. twos-compliment) integers, overflow more interesting.

Example: Addition in 4 bits.

$$\begin{array}{r} 1000 \text{ (carry bits)} \\ 1101 \\ + 0110 \\ \hline 10011 \end{array} \Rightarrow c_n \text{ is 1. Overflow?}$$

Addition Overflow (1/2)

Overflow occurs when arithmetic results in a number strictly larger than can fit in the predetermined number of bits.

- For *unsigned* integers, overflow is detected by c_n being 1.
- For *signed* (i.e. twos-compliment) integers, overflow more interesting.

Example: Addition in 4 bits.

$$\begin{array}{r} 1000 \text{ (carry bits)} \\ 1101 \\ + 0110 \\ \hline 10011 \end{array} \Rightarrow c_n \text{ is 1. Overflow?}$$

$$\begin{array}{r} -3 \\ + 6 \\ \hline 3 \end{array} \Rightarrow \begin{array}{l} \text{No overflow} \\ \text{Discard last carry bit} \end{array}$$

Addition Overflow (2/2)

In two's-complement when is there overflow?

- Most significant bit encodes a negative number in two's complement.
- If both operands are positive *and* $c_{n-1} \equiv 1$ then we have overflow.
- If one positive and one negative, overflow impossible.
 - ↳ Their sum is always closer to zero than either of the operands.
- If both operands are negative *and* $c_n \equiv 1$ then we have overflow.

$\begin{array}{r} \textcolor{red}{1}000 \Rightarrow \text{Overflow} \\ 0101 \\ +0110 \\ \hline 1011 \end{array}$	$\begin{array}{r} 1000 \\ +1000 \\ \hline \textcolor{red}{1}0000 \Rightarrow \text{Overflow} \end{array}$	$\begin{array}{r} 1000 \\ 1101 \\ + 0110 \\ \hline \textcolor{red}{1}0011 \Rightarrow \text{No overflow} \end{array}$
--	---	---

Overflow in two's complement: $c_n \text{ XOR } c_{n-1}$.

n -bit Subtractor (1/2)

n -bit subtractor: Subtract two n -bit numbers.

- We want $s = a - b$.
- Start with an n -bit adder.
- XOR b with a **control signal** for subtraction.
 - ↳ signal is 1 for subtraction, 0 for addition.

XOR works as conditional inverter.


↳ $A \text{ XOR } B \equiv C \implies \text{if } (B) \text{ then } \bar{A} \equiv C \text{ else } A \equiv C.$

A	B	$A \oplus B \equiv C$
0	0	0
0	1	1
1	0	1
1	1	0

n-bit Subtractor (2/2)

Control signal SUB acts as c_0 .

 - ↳ Recall: *signed negation*. Invert and add one.
- ↳ XOR does invert.



Outline


- 1 Combinational Circuits
- 2 Adders and Subtractors
- 3 MUX and DEMUX
- 4 Arithmetic Logic Units

Multiplexer

A **multiplexer** “mux” conditionally chooses among its inputs to set value of output.

- Uses **control signal** to control which input is chosen.
- Still no state, output depending only on inputs: input bits and control signal.

2-way multiplexer

 

If $s \equiv 0$ then $c \equiv a$.


If $s \equiv 1$ then $c \equiv b$.

Notice actual value of a and b have no effect on decision.

↳ 0 and 1 in multiplexer is not the *value* of a or b but the “index”.

2-way Multiplexer

 
How to encode this “if-then” behaviour without actual conditionals?



$$\begin{aligned}c &\equiv MUX(a, b, s) \\&\equiv \bar{s}a(b + \bar{b}) + sb(a + \bar{a}) \\&\equiv \bar{s}a + sb\end{aligned}$$

Note: $X \cdot (Y + \bar{Y})$ encodes “ X independent of what the value of Y is”.

4-way Multiplexer

 


$$\begin{aligned} e &\equiv \text{MUX}(a, b, c, d, S) \\ &\equiv \overline{s_1}\overline{s_0}a + \overline{s_1}s_0b \\ &\quad + s_1\overline{s_0}c + s_1s_0d \end{aligned}$$

The index of each input is now 0 through 3.

- Need 2 bits to choose among 4 inputs.
- Control signal's **bit-width** is now 2.

Big Data Multiplexer

 


Bit-width of input and output must match, but bit-width of *control signal* only determined by number of inputs to choose from.

Demultiplexer

Demultiplexer “demux” conditionally chooses among its outputs.

 - ↳ Opposite of MUX.
- ↳ Un-selected outputs are set to 0.



Outline

- 1 Combinational Circuits
- 2 Adders and Subtractors
- 3 MUX and DEMUX
- 4 Arithmetic Logic Units

Arithmetic Logic Unit

- An **ALU** is a black-box type circuit which can do many *different* arithmetic or logic operations on its inputs.
 - ↳ Not many at one time, but selectively acts as many.
- Depending on the implementation can do addition, subtraction, multiplication, division, logical AND, logical OR, shifting, etc.
- Use a control signal to choose which operation to perform.
- Essentially a big collection of MUX and combinational blocks for each operation.

Simple ALU Circuit


ALU depends on multiplexer

inputs.

control signal -

S_0

overflow

 

Optimizing ALU

Remember, every additional gate increases delay and space. Instead, optimize via the normal four step process:

- 1 Generate a truth table,
- 2 Get canonical form from truth table,
- 3 Simplify expression,
- 4 Make circuit.

Another option: programmable logic array.

Programmable Logic Array

A **programmable logic array** (PLA) directly

implements a truth table/canonical disjunctive normal form.

- Each AND row is a truth table row.
- Each OR column is one output bit.
- Each \oplus is a *programmable* (i.e. optional) AND gate (on the AND plane; OR gate on the OR plane) joining the input to the circuit.

