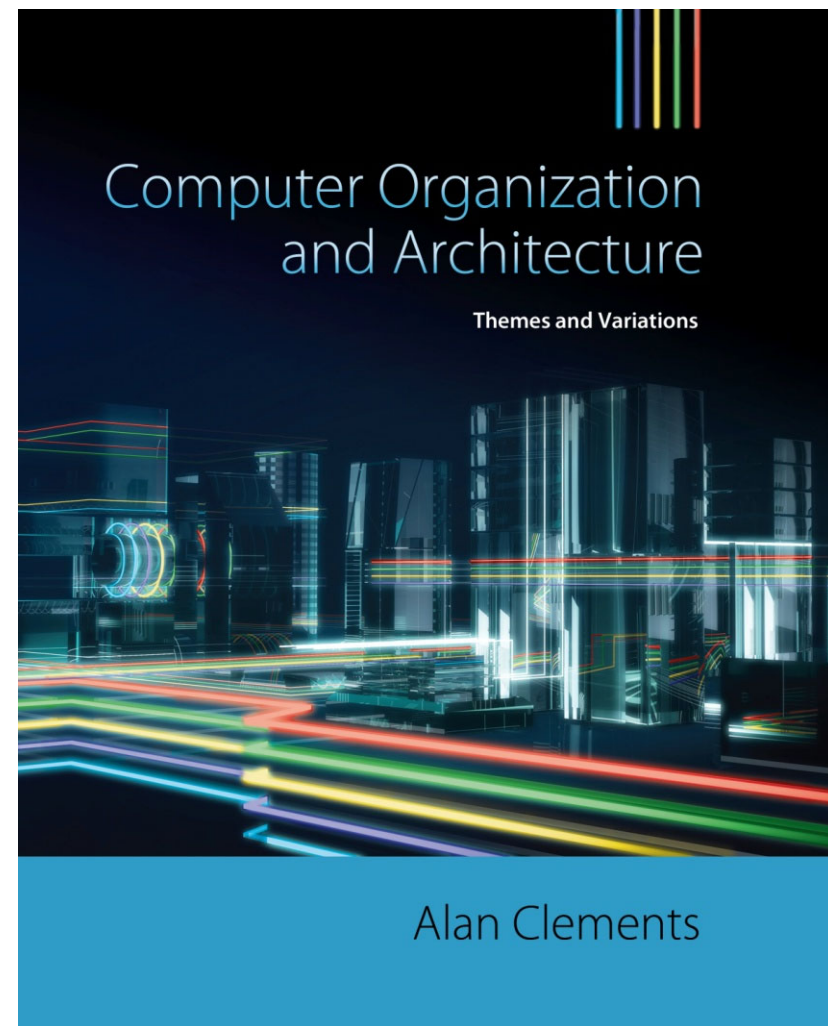


# Part 5

## CHAPTER 2

### Computer Arithmetic and Digital Logic



1

These slides are provided with permission from the copyright for CS2208 use only. The slides must not be reproduced or provided to anyone outside the class.

All downloaded copies of the slides are for personal use only.


Students must destroy these copies within 30 days after receiving the course's final assessment.

## More Example of a Digital Circuit

- Figure 2.21 describes a circuit with
  - four gates, labeled **G1**, **G2**, **G3** and **G4**.
  - three inputs **A**, **B**, and **X**, and
  - an output **C**.
  - It also has three intermediate logical values labeled **P**, **Q**, and **R**.
- We can **treat a gate as a processor** that operates on its inputs according to its logical function;
  - For example, the inputs to gate **G3** are **P** and **X**, and its output is **P · X**.
  - Because **P** = **A + B**, the output of **G3** is **(A + B) · X**.
  - Similarly, the output of gate **G4** is **R + Q**,
  - Because **R** = **(A + B) · X** and **Q** = **A · B**, the output of gate **G4** is **(A + B) · X + A · B**.

**FIGURE 2.21**

A circuit with four gates

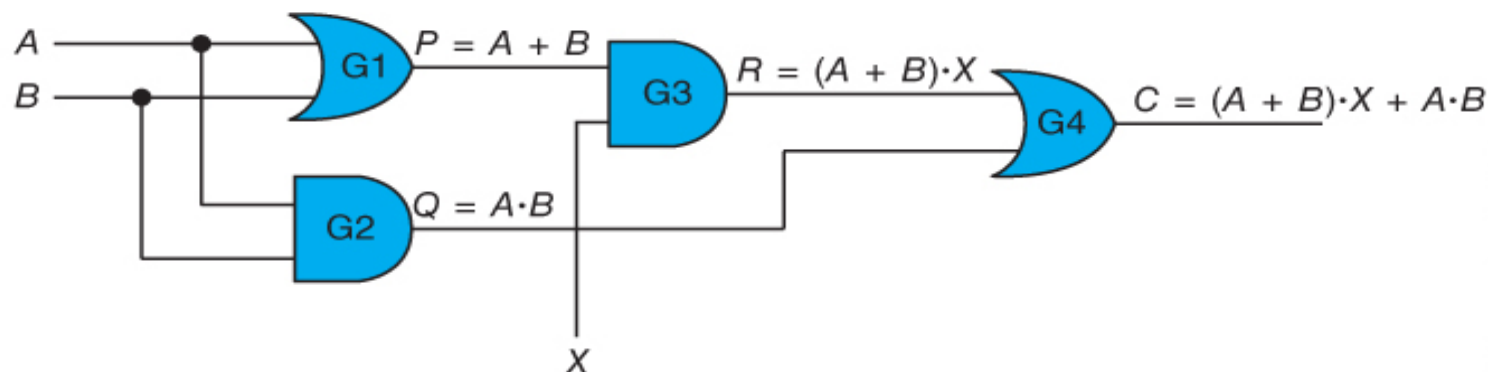

© Cengage Learning 2014

## More Example of a Digital Circuit


- Table 2.12 gives the truth table for Figure 2.21.
- Note that the *output corresponds to the carry out of a 3-bit adder*.

**TABLE 2.12** Truth Table for Figure 2.21

Inputs			Intermediate Values			Output
$X$	$A$	$B$	$P = A + B$	$Q = A \cdot B$	$R = (A + B) \cdot X$	$C = Q + R$
0	0	0	0	0	0	0
0	0	1	1	0	0	0
0	1	0	1	0	0	0
0	1	1	1	1	0	1
1	0	0	0	0	0	0
1	0	1	1	0	1	1
1	1	0	1	0	1	1
1	1	1	1	1	1	1

© Cengage Learning 2014

**FIGURE 2.21** A circuit with four gates

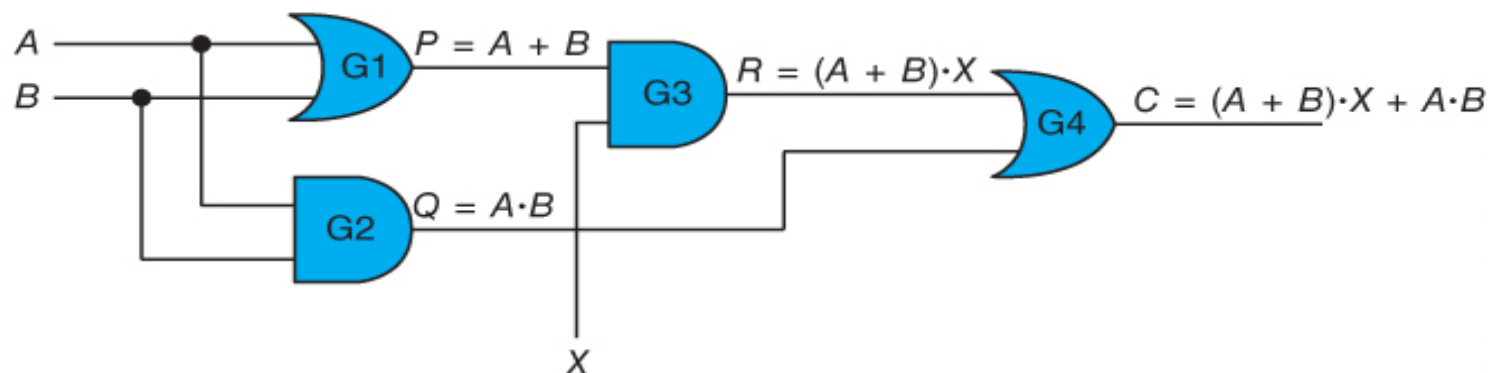

© Cengage Learning 2014

# The Half-Adder and Full-Adder

- ❑ Table 2.13 gives the truth table of a *half-adder* that adds bit **A** to bit **B** to get a **sum** and a **carry**. A single-bit full-adder is a logical circuit that performs an addition operation on three one-bit binary digits
- ❑ Figure 2.22 shows the possible structure of a two-bit adder.
  - The **sum** bit is generated by **XOR**ing the two inputs.
  - The **carry** bit is generated by **AND**ing the two inputs.

TABLE 2.13


Truth Table of a Half Adder

A	B	Sum	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

© Cengage Learning 2014

FIGURE 2.22

The two-bit adder (the half adder)

 

© Cengage Learning 2014

# Full-Adder Circuit

□ Figure 2.3 gives the possible circuit of a *one-bit full-adder*.

- Consists of *two half-adder* and a *one OR* gate


$$\begin{aligned} \text{Sum} &= (A \oplus B) \oplus C_{in} \leftarrow \text{Carry} \\ &= (A \cdot B + \bar{A} \cdot \bar{B}) \cdot C_{in} + (A \cdot \bar{B} + \bar{A} \cdot B) \cdot C_{in} \end{aligned}$$

$$C_{out} = A \cdot B + (A \oplus B) \cdot C_{in}$$

A	B	C <sub>in</sub>	Sum	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

FIGURE 2.23

The full adder

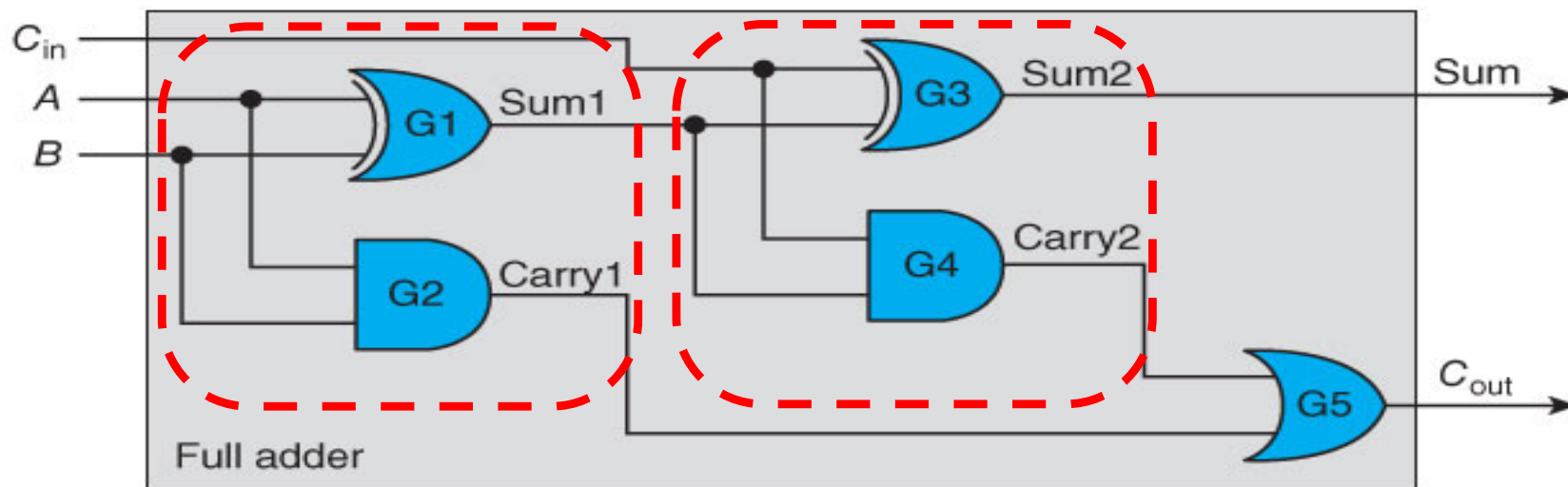

# Full-Adder Circuit

□ Figure 2.3 gives an alternative circuit of a *one-bit full-adder*.


$$\begin{aligned}\text{Sum} &= (A \oplus B) \oplus C_{in} \\ &= (A \cdot \bar{B} + \bar{A} \cdot B) \cdot \bar{C}_{in} + (A \cdot \bar{B} + \bar{A} \cdot B) \cdot C_{in}\end{aligned}$$

$$C_{out} = C_{in} \cdot A + A \cdot B + C_{in} \cdot B$$

A	B	C <sub>in</sub>	Sum	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**FIGURE 2.24**

Alternative full adder circuit

 

© Cengage Learning 2014

# Full-Adder Circuit

$$\text{Sum} = (A \oplus B) \oplus C$$

$$= (A \cdot \bar{B} + \bar{A} \cdot B) \cdot \bar{C} + \overline{(A \cdot \bar{B} + \bar{A} \cdot B)} \cdot C$$

Using De Morgan's law:  $\overline{X + Y} = \bar{X} \cdot \bar{Y}$

$$= (A \cdot \bar{B} + \bar{A} \cdot B) \cdot \bar{C} + (\overline{(A \cdot \bar{B})} \cdot \overline{(\bar{A} \cdot B)}) \cdot C$$

Using De Morgan's law:  $\overline{X \cdot Y} = \bar{X} + \bar{Y}$

$$= (A \cdot \bar{B} + \bar{A} \cdot B) \cdot \bar{C} + ((\bar{A} + \bar{\bar{B}}) \cdot (\bar{\bar{A}} + \bar{B})) \cdot C$$

Using property  $\bar{\bar{A}} = A$

$$= (A \cdot \bar{B} + \bar{A} \cdot B) \cdot \bar{C} + ((\bar{A} + B) \cdot (A + \bar{B})) \cdot C$$

Using Distributive law:  $X \cdot (Y + Z) = X \cdot Y + X \cdot Z$

$$= (A \cdot \bar{B} + \bar{A} \cdot B) \cdot \bar{C} + ((\bar{A} + B) \cdot A + (\bar{A} + B) \cdot \bar{B}) \cdot C$$

Using Commutative law:  $X \cdot Y = Y \cdot X$

$$= \bar{C} \cdot (A \cdot \bar{B} + \bar{A} \cdot B) + (A \cdot (\bar{A} + B) + \bar{B} \cdot (\bar{A} + B)) \cdot C$$

Using Distributive law:  $X \cdot (Y + Z) = X \cdot Y + X \cdot Z$

$$= (\bar{C} \cdot A \cdot \bar{B} + \bar{C} \cdot \bar{A} \cdot B) + ((A \cdot \bar{A} + A \cdot B) + (\bar{B} \cdot \bar{A} + \bar{B} \cdot B)) \cdot C$$

Using property  $\bar{X} \cdot X = 0$

$$= (\bar{C} \cdot A \cdot \bar{B} + \bar{C} \cdot \bar{A} \cdot B) + ((0 + A \cdot B) + (\bar{B} \cdot \bar{A} + 0)) \cdot C$$

Using inversion property:  $X + 0 = X$

$$= (\bar{C} \cdot A \cdot \bar{B} + \bar{C} \cdot \bar{A} \cdot B) + (A \cdot B + \bar{B} \cdot \bar{A}) \cdot C$$

Using Commutative law:  $X \cdot Y = Y \cdot X$

$$= (\bar{C} \cdot A \cdot \bar{B} + \bar{C} \cdot \bar{A} \cdot B) + C \cdot (A \cdot B + \bar{B} \cdot \bar{A})$$

Using Distributive law:  $X \cdot (Y + Z) = X \cdot Y + X \cdot Z$

$$= \bar{C} \cdot A \cdot \bar{B} + \bar{C} \cdot \bar{A} \cdot B + C \cdot A \cdot B + C \cdot \bar{B} \cdot \bar{A}$$

Using Commutative law:  $X \cdot Y = Y \cdot X$

$$= A \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot \bar{C} + A \cdot B \cdot C + \bar{A} \cdot \bar{B} \cdot C$$

A	B	C	Sum
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



# Full-Adder Circuit

$$C_{out} = (A + B) \cdot C + A \cdot B$$

$$C_{out} = C \cdot A + A \cdot B + C \cdot B$$

$$C_{out} = A \cdot B + (A \oplus B) \cdot C$$

$$C_{out} = A \cdot B + (A \cdot \bar{B} + \bar{A} \cdot B) \cdot C$$

*Using Distributive law*

$$C_{out} = A \cdot B + A \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot C$$

*Using Distributive law*

$$C_{out} = A \cdot (B + \bar{B} \cdot C) + \bar{A} \cdot B \cdot C$$

*Using*  $X + \bar{X} \cdot Y = X + Y$

$$C_{out} = A \cdot (B + C) + \bar{A} \cdot B \cdot C$$

*Using Distributive law*

$$C_{out} = A \cdot B + A \cdot C + \bar{A} \cdot B \cdot C$$

*Using Distributive law*

$$C_{out} = A \cdot B + (A + \bar{A} \cdot B) \cdot C$$

*Using*  $X + \bar{X} \cdot Y = X + Y$

$$C_{out} = A \cdot B + (A + B) \cdot C$$

*Using Distributive law*

$$C_{out} = A \cdot B + A \cdot C + B \cdot C$$

*Using Commutative law*

$$C_{out} = C \cdot A + A \cdot B + C \cdot B$$

*Using Commutative law:*

$$C_{out} = A \cdot C + B \cdot C + A \cdot B$$

*Using Distributive law*

$$C_{out} = (A + B) \cdot C + A \cdot B$$

*From Figure 2.21*

*From Figure 2.24*

*From Figure 2.23*

A	B	C	C <sub>out</sub>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

*As in Figure 2.24*

*As in Figure 2.21*




# Full-Adder

- ❑ We need  $m$  *full-adder* circuits to add two  $m$ -bit words *in parallel* as Figure 2.25 demonstrates.
- ❑ The  $m_i$  *full-adder* adds bit  $a_i$  to bit  $b_i$ , together with a *carry-in* from the stage on its right, to produce a *sum* $_i$  and a *carry-out* to the stage on its left.

**FIGURE 2.25**

The parallel adder

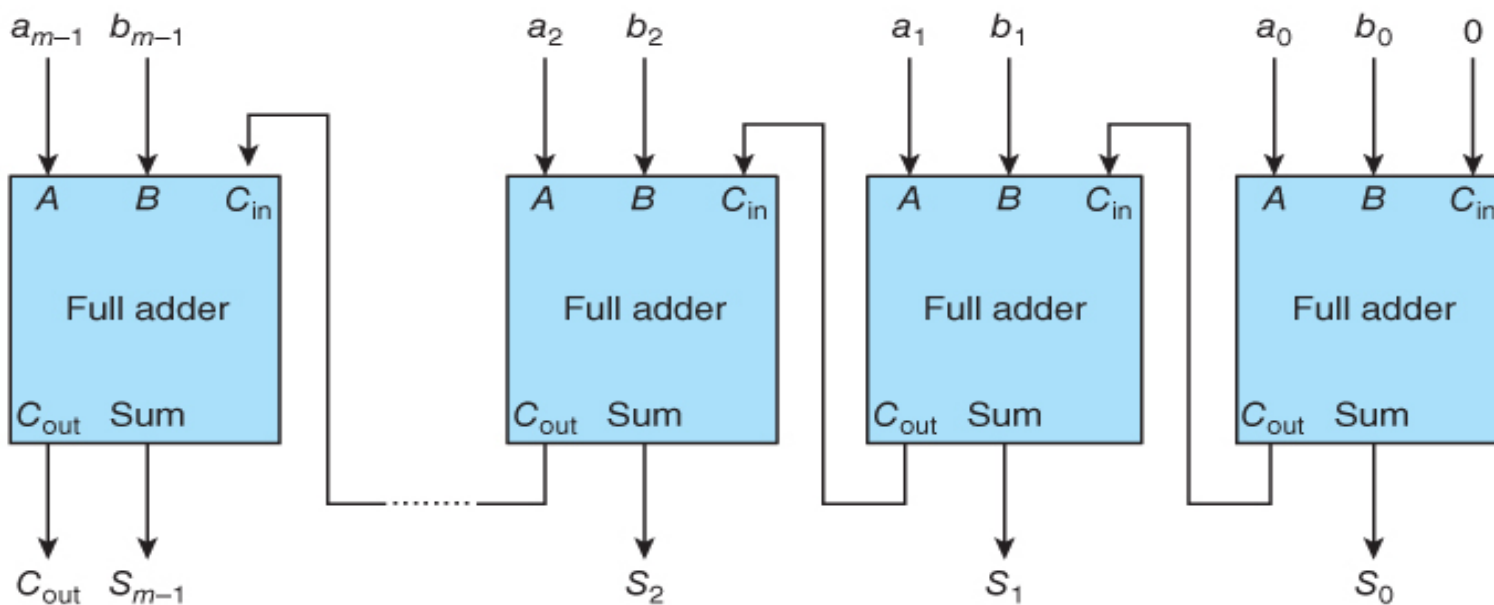


© Cengage Learning 2014

# Full-Adder

- ❑ This circuit is called a parallel-adder because all the bits of the two words to be added are presented to it at the same time.
- ❑ The circuit is *not truly parallel* because bit  $s_i$  cannot be correctly produced until the *carry-in<sub>i</sub>* bit has been calculated by the *previous stage*.
- ❑ This is a *ripple through* adder because addition is not complete until the carry bit has *rippled* through the circuit.
- ❑ *True parallel-adders* use high-speed *look-ahead carry* circuits to produce all carry bits at once, hence speeding up the addition operation.


**FIGURE 2.25** The parallel adder

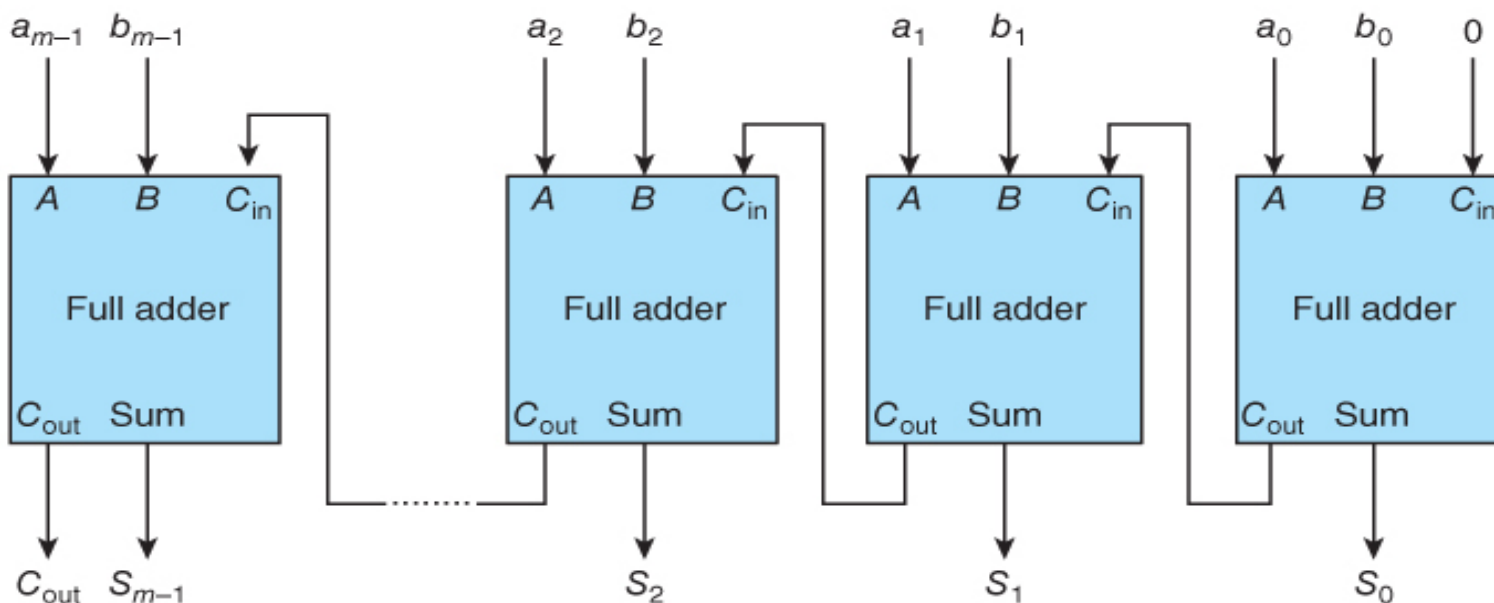

# Programmable Inverter

a	X	$a \oplus X$
0	0	0
0	1	1
1	0	1
1	1	0

**FIGURE 2.26** The programmable inverter

 


The outputs are copies of the respective inputs if  $X = 0$ , and the complements of the inputs if  $X = 1$

# Full-Adder/Subtractor

FIGURE 2.27

The adder/subtractor

 


# The Decoder

- ❑ Figure 2.29 has **three** inputs A, B, and C, and **eight** outputs Y0 to Y7.
- ❑ The **three** inverters generate the complements of the inputs A, B, and C.
- ❑ Each of the **eight AND** gates is connected to **three** of the six lines .
  - each of the **three** variables appear in either its true or complemented form.

FIGURE 2.28

Application of a decoder

 


A **decoder** is combinational logic circuit that converts binary information from the  $n$ -bits coded input to a maximum of  $2^n$  unique outputs.

# The Decoder

TABLE 2.15 The Decoder

Inputs			Outputs							
A	B	C	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	Y <sub>4</sub>	Y <sub>5</sub>	Y <sub>6</sub>	Y <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


FIGURE 2.28 Application of a decoder

 


A *decoder* is combinational logic circuit that converts binary information from the n-bits coded input to a maximum of 2<sup>n</sup> unique outputs.
 
# The Multiplexer

- ❑ When  $C = 0$ , the output is A
- ❑ When  $C = 1$ , the output is B
- ❑ C works as a selector to select either A or B to go



 Alternative representation of the two-input multiplexer



Truth table

C	A	B
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1


S
0
0
1
1
0
1
0
1

A **multiplexer** is combinational logic circuit that has up to  $2^n$  binary input lines and  $n$  select lines, where the  $n$  select-lines are used to forward one of the input values to the output line.




# The Multiplexer

- ❑ When  $C = 0$ , the output is A
- ❑ When  $C = 1$ , the output is B
- ❑ C works as a selector to select either A or B to go

 

**FIGURE 2.29** The two-input multiplexer and its truth table

 



**Truth table**

C	A	B	P	Q	R	S
0	0	0	1	1	1	0
0	0	1	1	1	1	0
0	1	0	1	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	1	0
1	0	1	0	1	0	1
1	1	0	0	1	1	0
1	1	1	0	1	0	1

© Cengage Learning 2014

A **multiplexer** is combinational logic circuit that has up to  $2^n$  binary input lines and  $n$  select lines, where the  $n$  select-lines are used to forward one of the input values to the output line.

# The Multiplexer

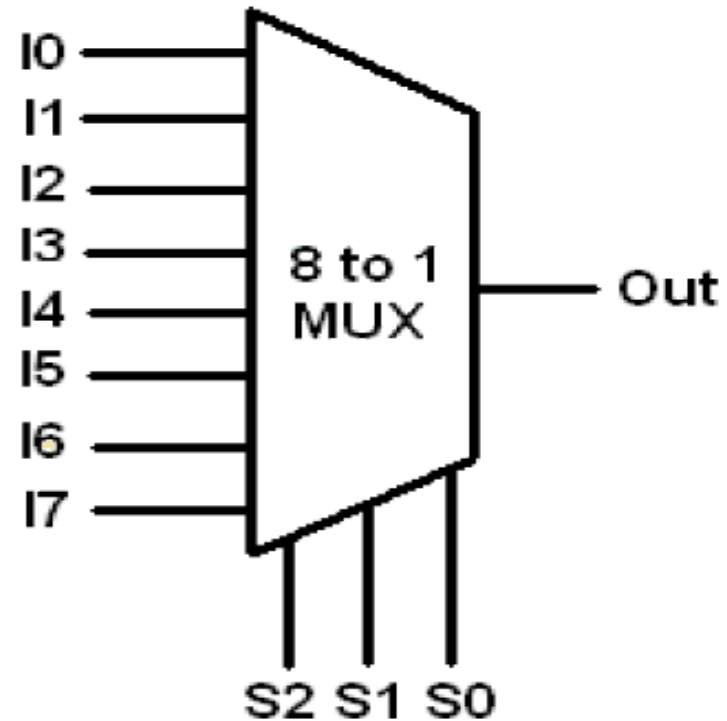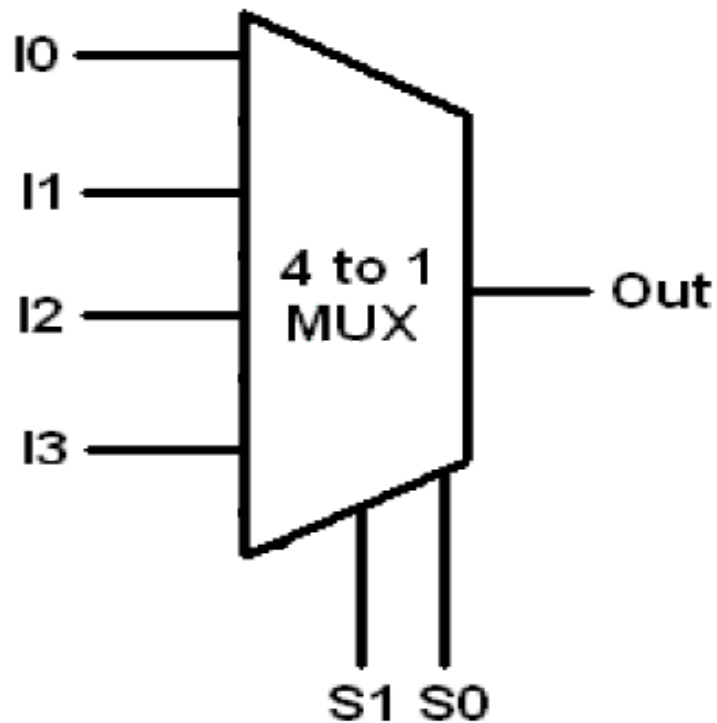

A **multiplexer** is combinational logic circuit that has up to  $2^n$  binary input lines and  $n$  select lines, where the  $n$  select-lines are used to forward one of the input values to the output line.

## One Bit of an ALU

- ❑ This diagram describes **one-bit of a primitive ALU** that can perform **five operations** on bits A and B (**XOR**, **AND**, **OR**, **NOT A** and **NOT B**).
- ❑ The function to be performed is determined by the **three-bit control signal**  $F_2, F_1, F_0$ .
- ❑ The five functions are generated by the five gates on the left.
- ❑ On the right, five **AND** gates are used to gate the selected function to an **OR** gate to produce the output.

