

These slides are being provided with permission from the copyright for CS2208 use only. The slides must not be reproduced or provided to anyone outside of the class.

All download copies of the slides and/or lecture recordings are for personal use only. Students must destroy these copies within 30 days after receipt of final course evaluations.



Tutorial 06: Combinational Circuits

Computer Science Department

CS2208: Introduction to Computer Organization and Architecture

Fall 2022-2023

Instructor: Mahmoud R. El-Sakka

Office: MC-419


Email: elsakka@csd.uwo.ca

Phone: 519-661-2111 x86996

Gates

■ Gates

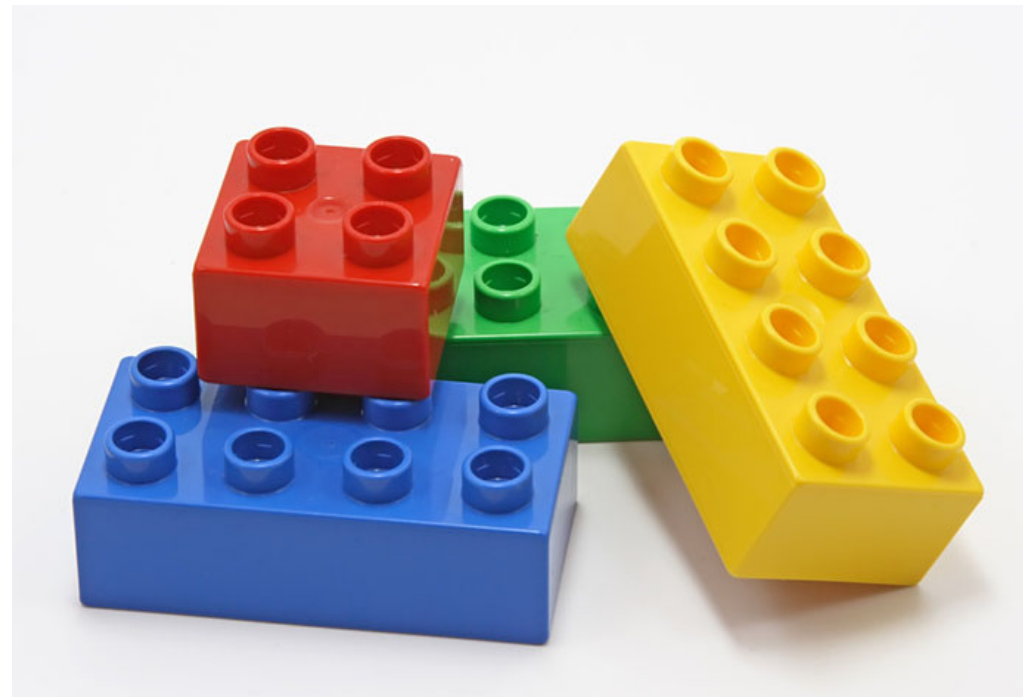
- Are our building blocks when considering hardware realization
- Can be used to build combinational circuits, as well as latches, flip-flops, and sequential circuits
- Come in many flavors, including
 - AND
 - OR
 - NOT
 - NAND (Not AND)
 - NOR (Not OR)
 - XOR



Gates


■ AND:

- True only when all input are true

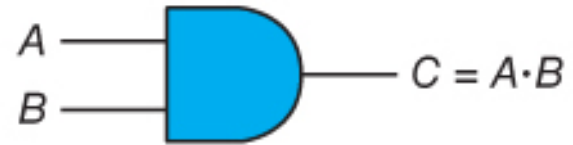


■ OR:

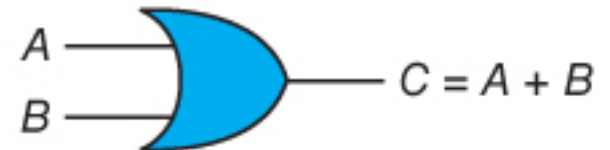- True only when at least one input is true




■ NOT:

- Complementing the input Boolean value

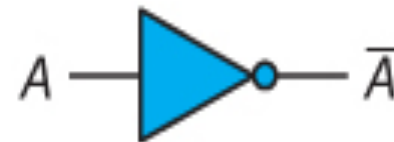


■ NAND:

- The complement of an AND result

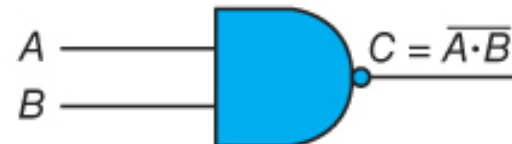

■ NOR:

- The complement of an OR result

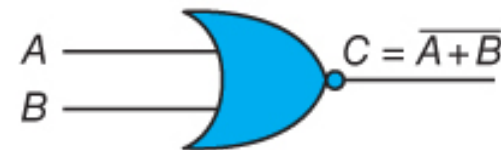


■ XOR:

- True only when an odd number of inputs are true



Example 1


X ₀	X ₁	X ₂	X ₃	P	S	Q	T	R	C ₀	C ₁	C ₂	C ₃	F
0	0	0	0	0	1	0	1	1	B A C = A + B				
0	0	0	1	1	0	1	0	0	0	0	0		
0	0	1	0	1	0	1	0	1	0	1	1		
0	0	1	1	1	0	1	0	0	1	0	1		
0	1	0	0	0	1	1	0	1					
0	1	0	1	1	0	1	0	0	A	Ā			
0	1	1	0	1	0	1	0	1	1	0			
0	1	1	1	1	0	1	0	0	0	1			
1	0	0	0	0	1	0	1	1					
1	0	0	1	1	0	1	0	0					
1	0	1	0	1	0	1	0	1					
1	0	1	1	1	0	1	0	0					
1	1	0	0	0	1	1	0	1					
1	1	0	1	1	0	1	0	0					
1	1	1	0	1	0	1	0	1					
1	1	1	1	1	0	1	0	0					

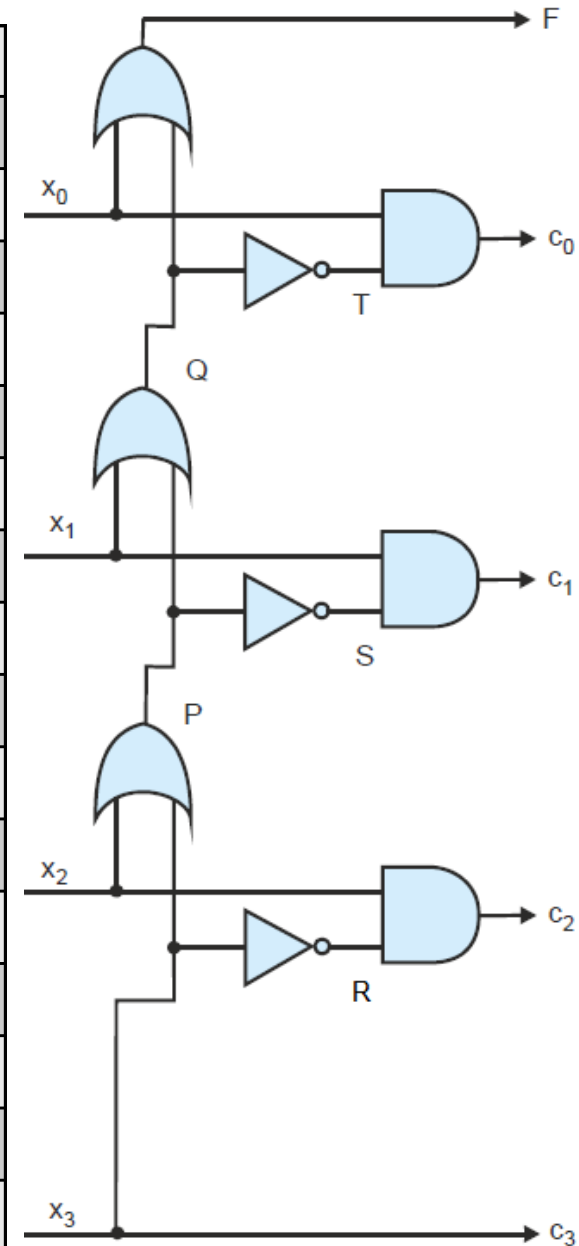

Example 1

X_0	X_1	X_2	X_3	P	S	Q	T	R	C_0	C_1	C_2	C_3	F
0	0	0	0	0	1	0	1	1	0	0			
0	0	0	1	1	0	1	0	0	0	0			
0	0	1	0	1	0	1	0	1	0	0			
0	0	1	1	1	0	1	0	0	0	0			
0	1	0	0	0	1	1	0	1	0	1			
0	1	0	1	1	0	1	0	0	0	0			
0	1	1	0	1	0	1	0	1	0	0			
0	1	1	1	1	0	1	0	0	0	0			
1	0	0	0	0	1	0	1	1	1	0			
1	0	0	1	1	0	1	0	0	0	0			
1	0	1	0	1	0	1	0	1	0	0			
1	0	1	1	1	0	1	0	0	0	0			
1	1	0	0	0	1	1	0	1	0	1			
1	1	0	1	1	0	1	0	0	0	0			
1	1	1	0	1	0	1	0	1	0	0			
1	1	1	1	1	0	1	0	0	0	0			


B	A	$C = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

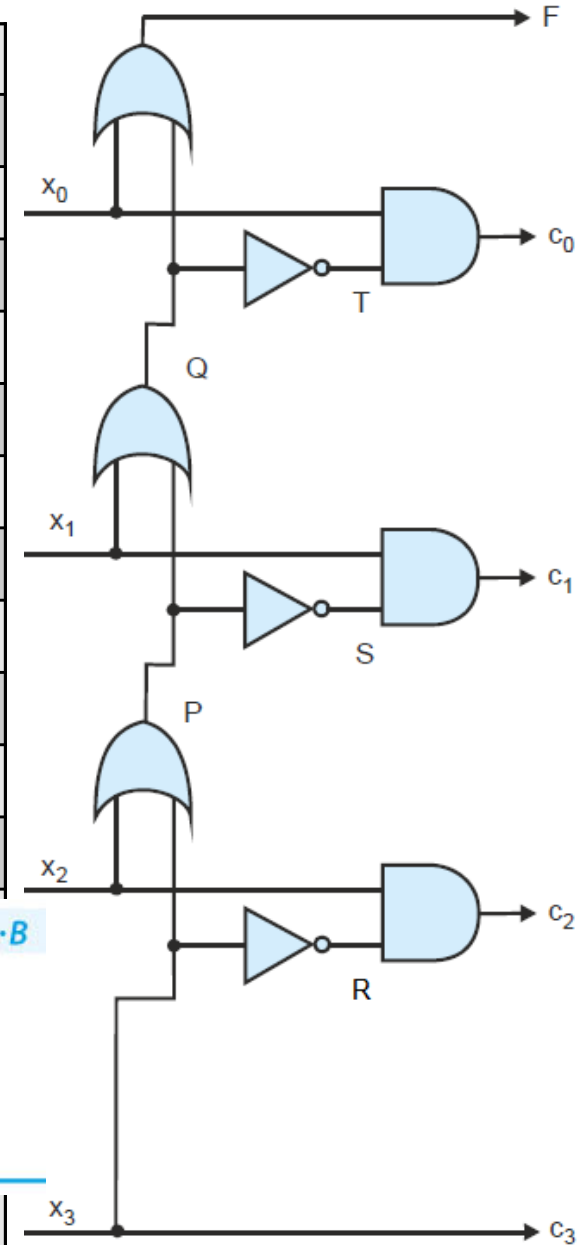

Example 1

X_0	X_1	X_2	X_3	P	S	Q	T	R	C_0	C_1	C_2	C_3	F
0	0	0	0	0	1	0	1	1	0	0	0	0	
0	0	0	1	1	0	1	0	0	0	0	0	1	
0	0	1	0	1	0	1	0	1	0	0	1	0	
0	0	1	1	1	0	1	0	0	0	0	0	1	
0	1	0	0										
0	1	0	1										
0	1	1	0										
0	1	1	1										
1	0	0	0	0	1	0	1	1	1	0	0	0	
1	0	0	1	1	0	1	0	0	0	0	0	1	
1	0	1	0	1	0	1	0	1	0	0	1	0	
1	0	1	1	1	0	1	0	0	0	0	0	1	
1	1	0	0	0	1	1	0	1	0	1	0	0	
1	1	0	1	1	0	1	0	0	0	0	0	1	
1	1	1	0	1	0	1	0	1	0	0	1	0	
1	1	1	1	1	0	1	0	0	0	0	0	1	


B	A	$C = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

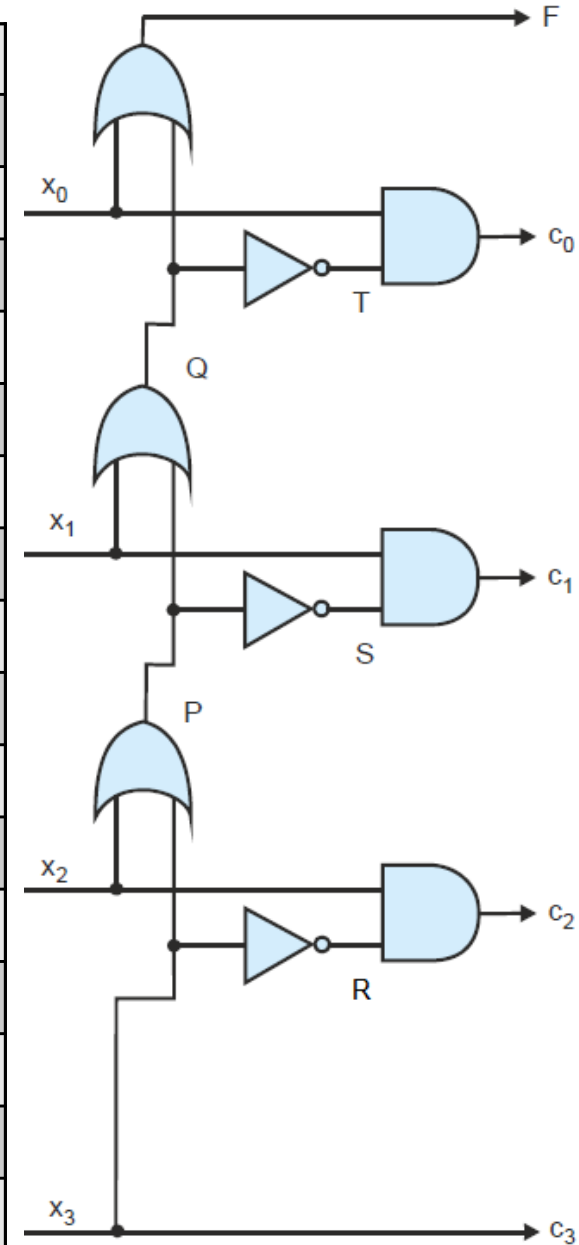

Example 1

X_0	X_1	X_2	X_3	P	S	Q	T	R	C_0	C_1	C_2	C_3	F
0	0	0	0	0	1	0	1	1	0	0	0	0	0
0	0	0	1	1	0	1	0	0	0	0	0	1	1
0						1	0	1	0	0	1	0	1
0						1	0	0	0	0	0	1	1
0						1	0	1	0	1	0	0	1
0						1	0	0	0	0	0	1	1
0						1	0	1	0	0	1	0	1
0	1	1	1	1	0	1	0	0	0	0	0	1	1
1	0	0	0	0	1	0	1	1	1	0	0	0	1
1	0	0	1	1	0	1	0	0	0	0	0	1	1
1	0	1	0	1	0	1	0	1	0	0	1	0	1
1	0	1	1	1	0	1	0	0	0	0	0	1	1
1	1	0	0	0	1	1	0	1	0	1	0	0	1
1	1	0	1	1	0	1	0	0	0	0	0	1	1
1	1	1	0	1	0	1	0	1	0	0	1	0	1
1	1	1	1	1	0	1	0	0	0	0	0	1	1


B	A	$C = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

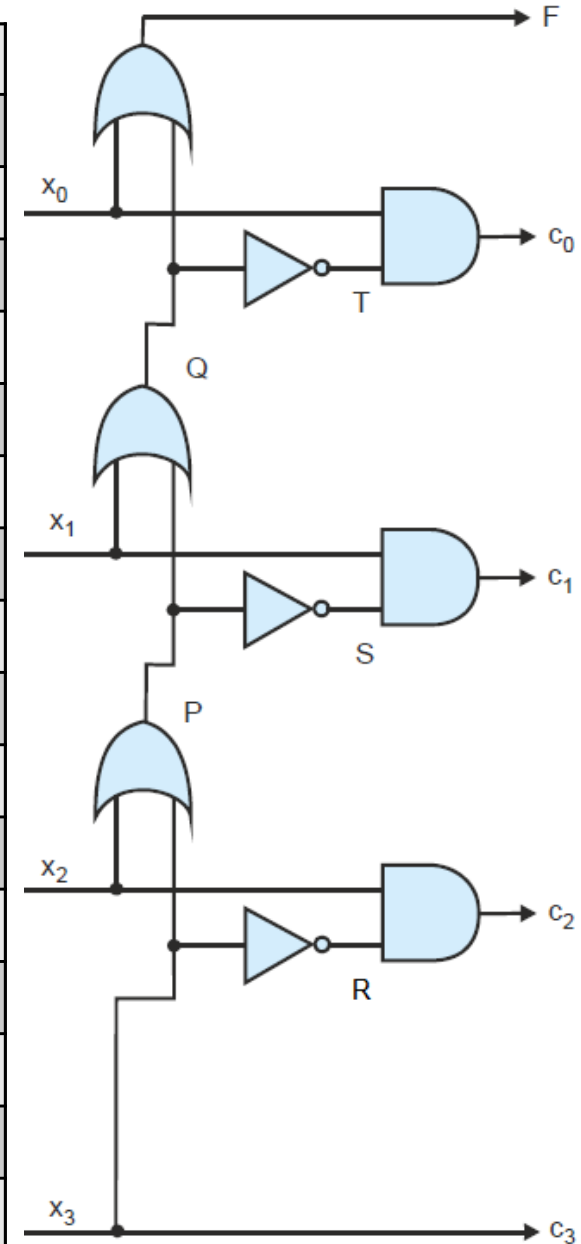

Example 1


X_0	X_1	X_2	X_3	P	S	Q	T	R	C_0	C_1	C_2	C_3	F
0	0	0	0	0	1	0	1	1	0	0	0	0	0
0	0	0	1	1	0	1	0	0	0	0	0	1	1
0	0	1	0	1	0	1	0	1	0	0	1	0	1
0	0	1	1	1	0	1	0	0	0	0	0	1	1
0	1	0	0	0	1	1	0	1	0	1	0	0	1
0	1	0	1	1	0	1	0	0	0	0	0	1	1
0	1	1	0	1	0	1	0	1	0	0	1	0	1
0	1	1	1	1	0	1	0	0	0	0	0	1	1
1	0	0	0	0	1	0	1	1	1	0	0	0	1
1	0	0	1	1	0	1	0	0	0	0	0	1	1
1	0	1	0	1	0	1	0	1	0	0	1	0	1
1	0	1	1	1	0	1	0	0	0	0	0	1	1
1	1	0	0	0	1	1	0	1	0	1	0	0	1
1	1	0	1	1	0	1	0	0	0	0	0	1	1
1	1	1	0	1	0	1	0	1	0	0	1	0	1
1	1	1	1	1	0	1	0	0	0	0	0	1	1

- $P = X_2 + X_3$
- $S = \overline{P} = \overline{(X_2 + X_3)} = \overline{X_2} \cdot \overline{X_3}$ (De Morgan law)
- $Q = X_1 + P = X_1 + X_2 + X_3$
- $T = \overline{Q} = \overline{X_1 + X_2 + X_3} = \overline{X_1} \cdot \overline{X_2} \cdot \overline{X_3}$ (De Morgan law)
- $R = \overline{X_3}$
- $C_0 = X_0 \cdot T = X_0 \cdot \overline{X_1} \cdot \overline{X_2} \cdot \overline{X_3}$
- $C_1 = X_1 \cdot S = X_1 \cdot \overline{X_2} \cdot \overline{X_3}$
- $C_2 = X_2 \cdot R = X_2 \cdot \overline{X_3}$
- $C_3 = X_3$
- $F = X_0 + Q = X_0 + X_1 + X_2 + X_3$

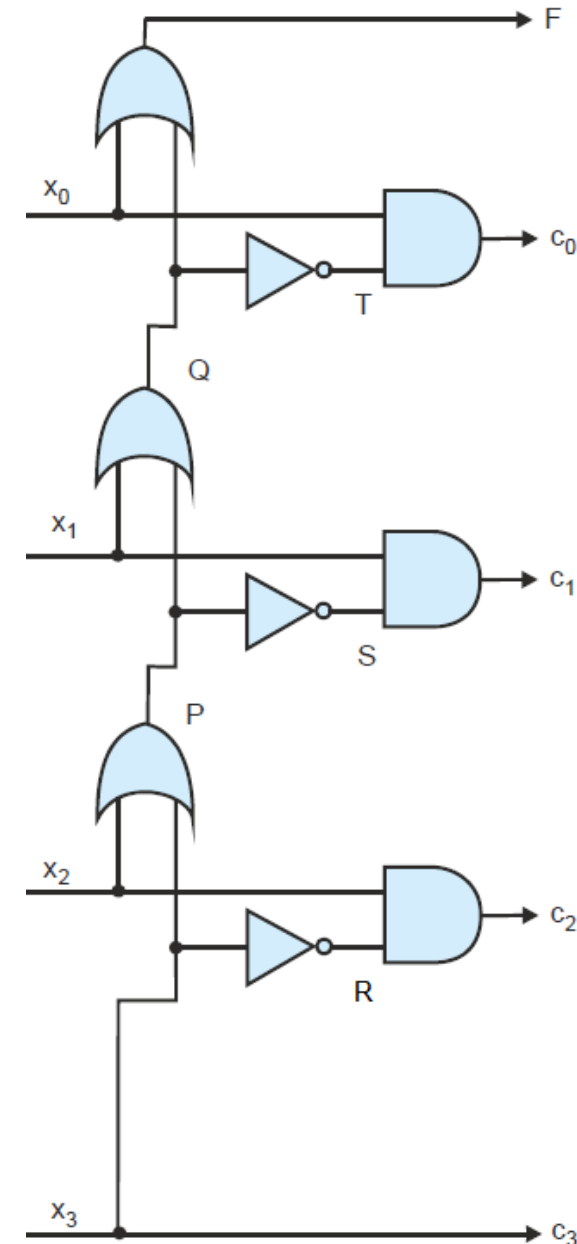


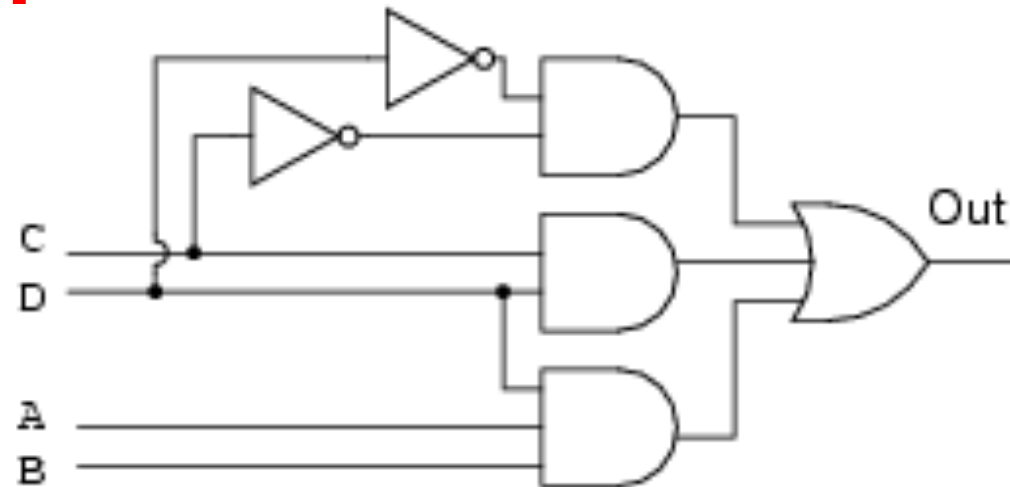Example 2

- $out = \overline{C} \overline{D} + CD + ABD$
- $out = \overline{\overline{\overline{C} \overline{D} + CD + ABD}}$
- $out = \overline{(\overline{\overline{C} \overline{D}} \cdot \overline{CD} \cdot \overline{ABD})}$








- An inverter can be also replaced by a NAND gate, as $\overline{X} \cdot \overline{X} = \overline{X}$
- The sum-of-products can be implemented by NAND gates only.

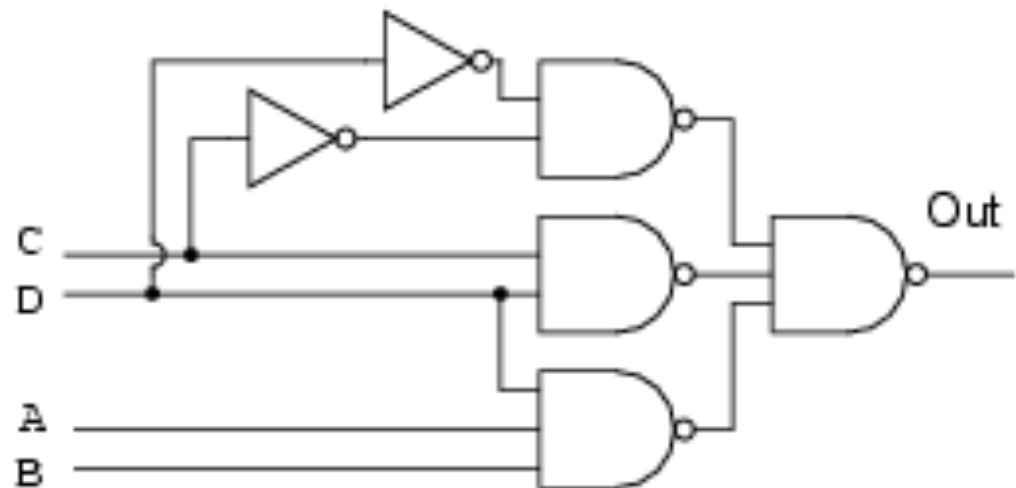



Example 2

- $out = \overline{C} \overline{D} + CD + ABD$
- $out = \overline{\overline{\overline{C} \overline{D} + CD + ABD}}$
- $out = \overline{(\overline{\overline{C} \overline{D}} \cdot \overline{CD} \cdot \overline{ABD})}$

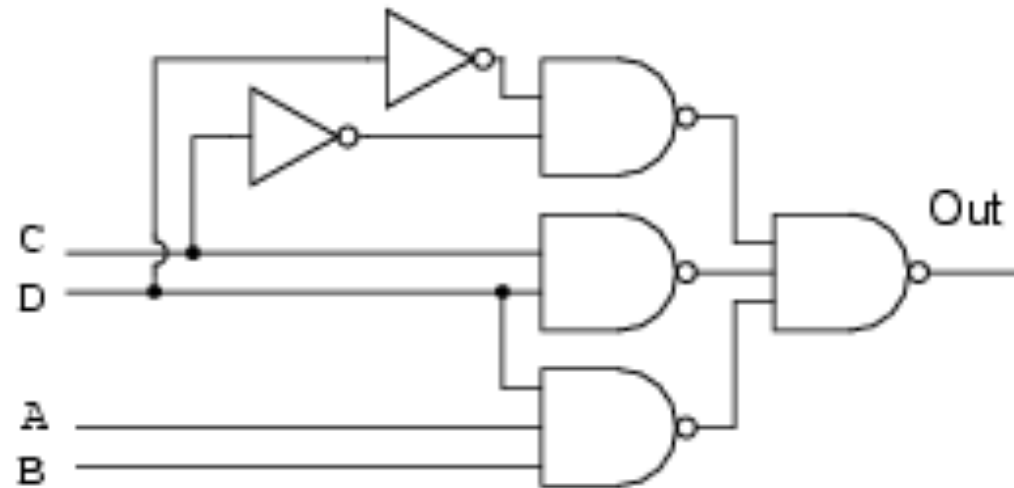
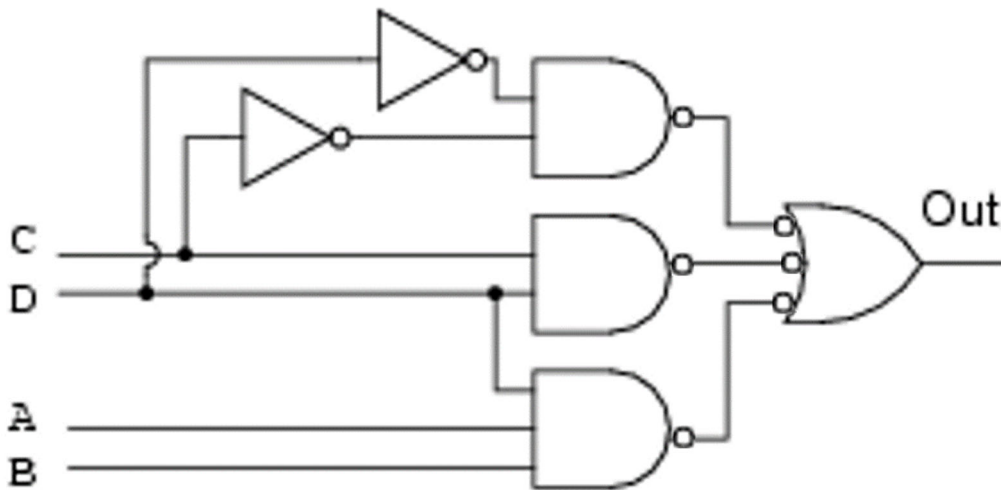
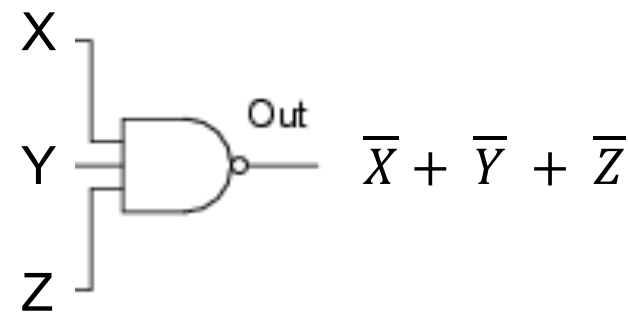
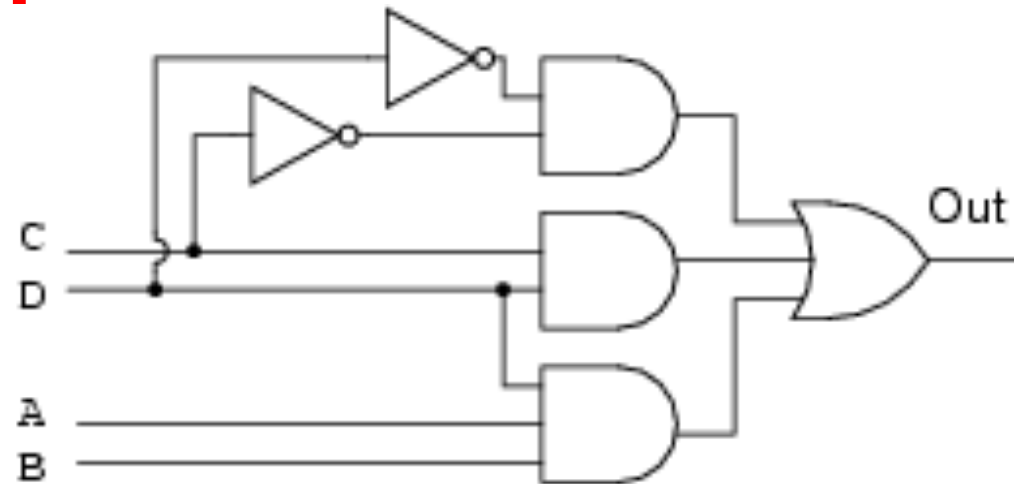
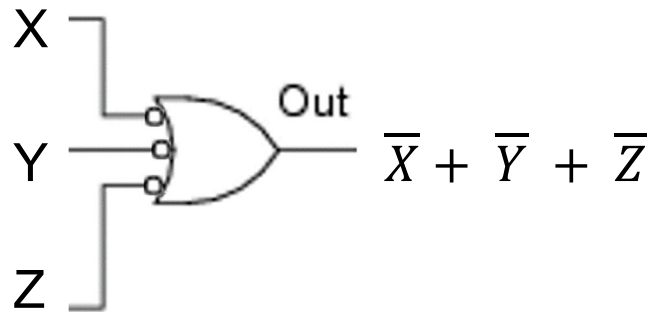


Example 3

- $out = (B + C + \overline{D}) \cdot (A + C + \overline{D}) \cdot (\overline{C} + D)$
- $out = \overline{\overline{(B + C + \overline{D}) \cdot (A + C + \overline{D}) \cdot (\overline{C} + D)}}$
- $out = \overline{((\overline{B + C + \overline{D}}) + (\overline{A + C + \overline{D}}) + (\overline{\overline{C} + D}))}$
- An inverter can be also replaced by a NOR gate, as $\overline{X + X} = \overline{X}$
- The product-of-sums can be implemented by NOR gates only.

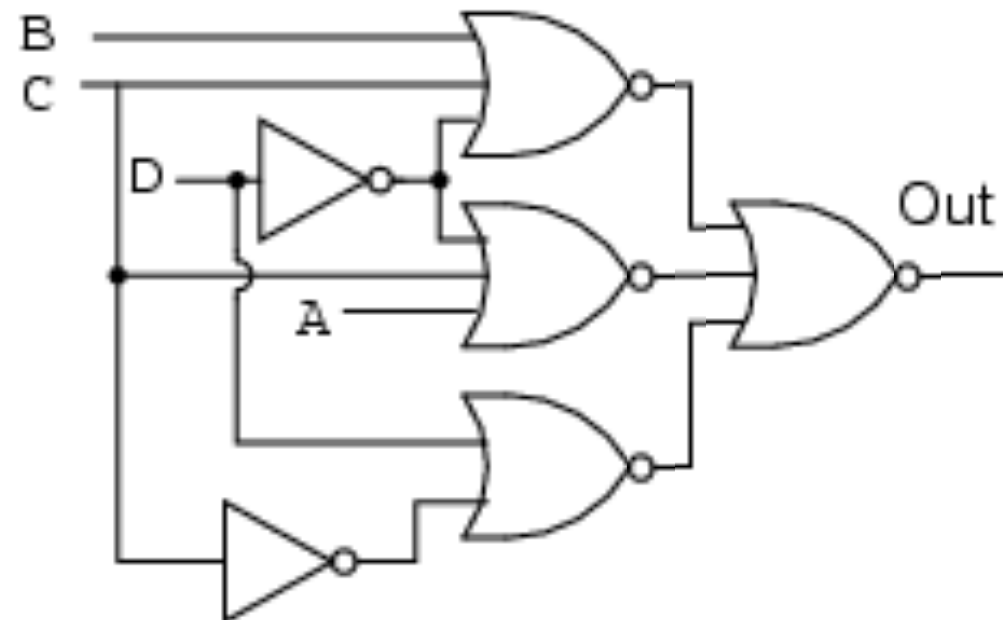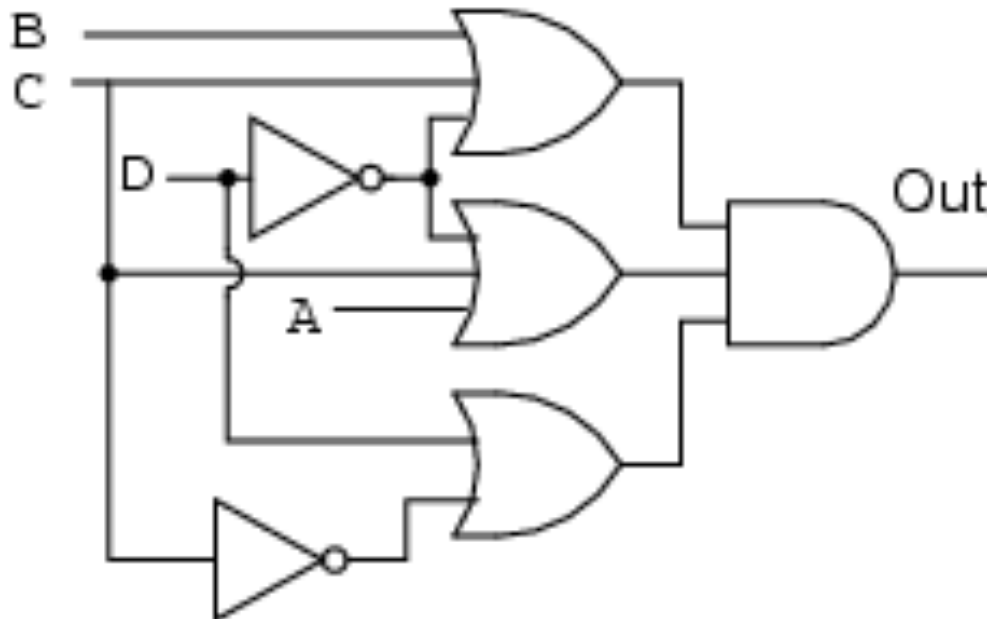


Example 3

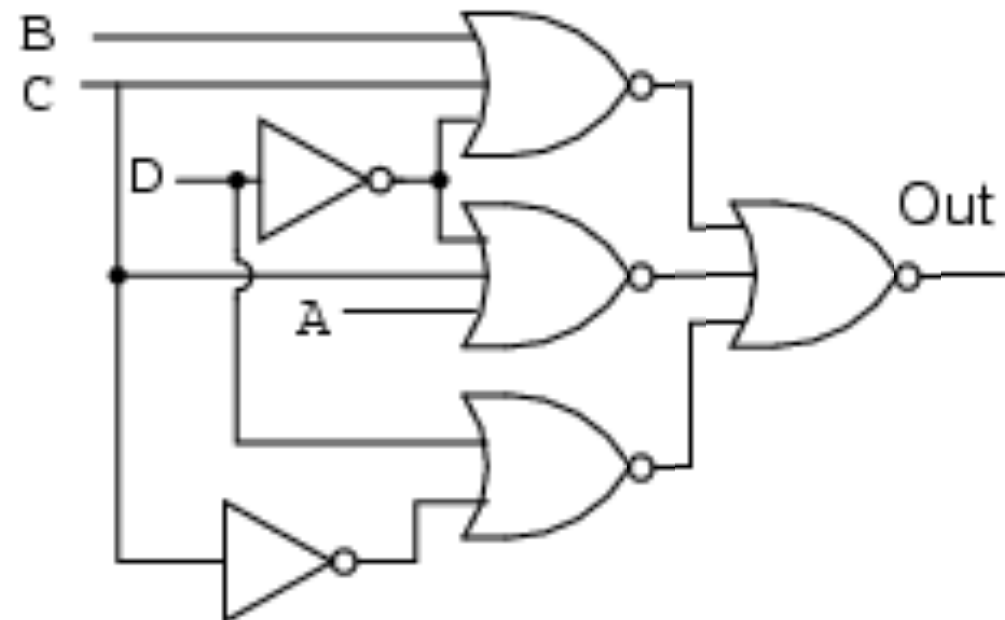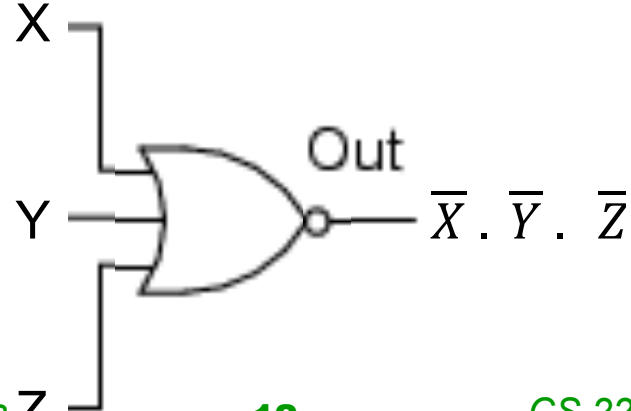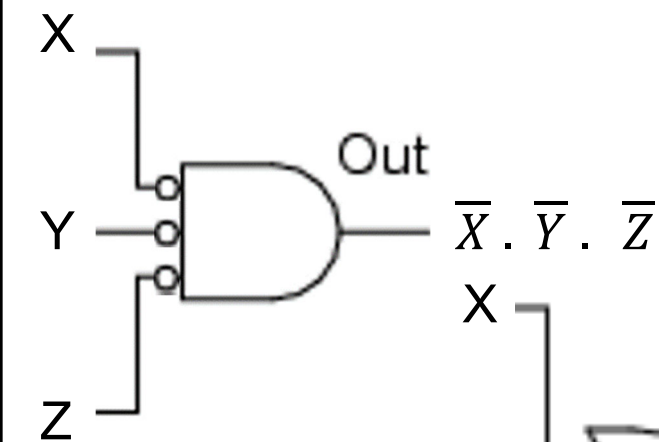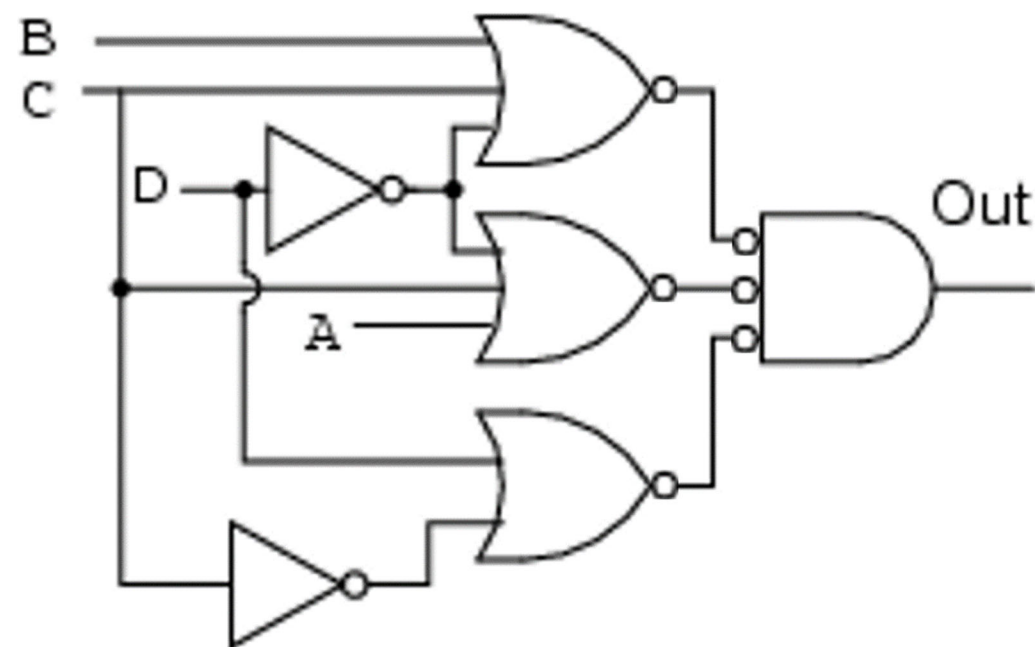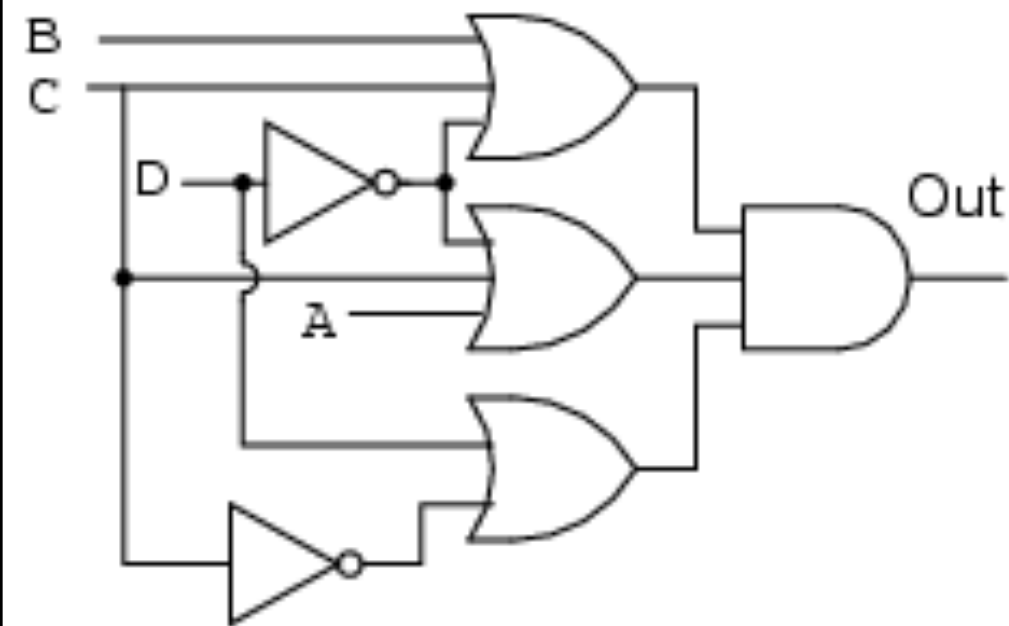

Example 4

$$P = \bar{A}$$

A	B	C	D	P	Q	R	S	T	F	G
0	0	0	0	1						
0	0	0	1	1						
0	0	1	0	1						
0	0	1	1	1						
0	1	0	0	1						
0	1	0	1	1						
0	1	1	0	1						
0	1	1	1	1						
1	0	0	0	0						
1	0	0	1	0						
1	0	1	0	0						
1	0	1	1	0						
1	1	0	0	0						
1	1	0	1	0						
1	1	1	0	0						
1	1	1	1	0						

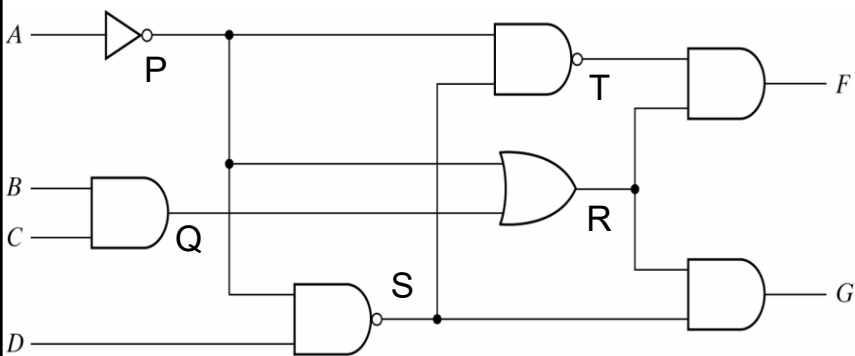


Example 4

A	B	C	D	P	Q	R	S	T	F	G
0	0	0	0	1	0					
0	0	0	1	1	0					
0	0	1	0	1	0					
0	0	1	1	1	0					
0	1	0	0	1	0					
0	1	0	1	1	0					
0	1	1	0	1	1					
0	1	1	1	1	1					
1	0	0	0	0	0					
1	0	0	1	0	0					
1	0	1	0	0	0					
1	0	1	1	0	0					
1	1	0	0	0	0					
1	1	0	1	0	0					
1	1	1	0	0	1					
1	1	1	1	0	1					

$$P = \bar{A}$$

$$Q = B \cdot C$$

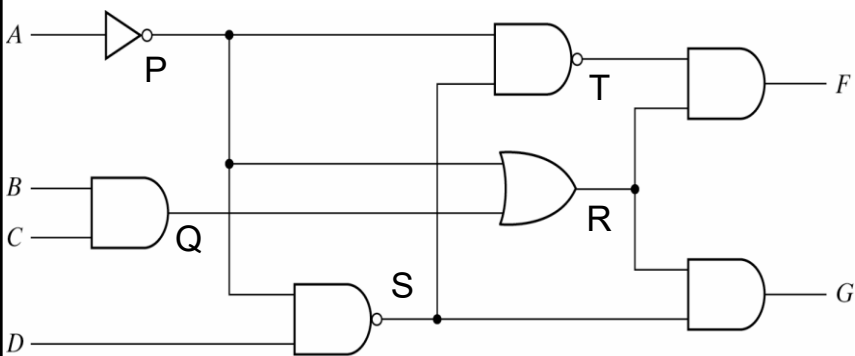


Example 4

A	B	C	D	P	Q	R	S	T	F	G
0	0	0	0	1	0	1				
0	0	0	1	1	0	1				
0	0	1	0	1	0	1				
0	0	1	1	1	0	1				
0	1	0	0	1	0	1				
0	1	0	1	1	0	1				
0	1	1	0	1	1	1				
0	1	1	1	1	1	1				
1	0	0	0	0	0	0				
1	0	0	1	0	0	0				
1	0	1	0	0	0	0				
1	0	1	1	0	0	0				
1	1	0	0	0	0	0				
1	1	0	1	0	0	0				
1	1	1	0	0	1	1				
1	1	1	1	0	1	1				

$$P = \bar{A}$$

$$Q = B \cdot C$$

$$R = P + Q = \bar{A} + B \cdot C$$

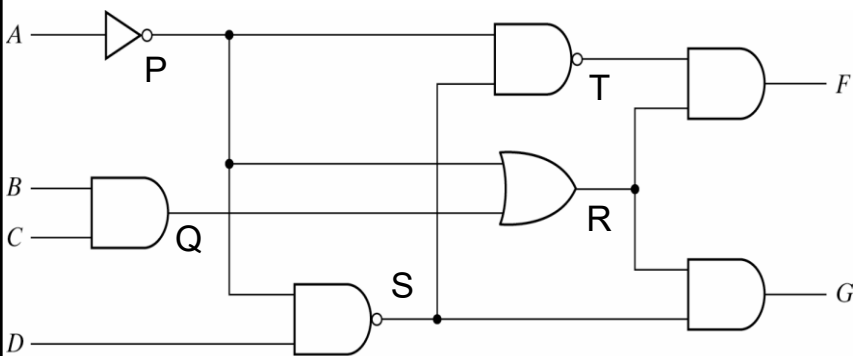

Example 4


A	B	C	D	P	Q	R	S	T	F	G
0	0	0	0	1	0	1	1			
0	0	0	1	1	0	1	0			
0	0	1	0	1	0	1	1			
0	0	1	1	1	0	1	0			
0	1	0	0	1	0	1	1			
0	1	0	1	1	0	1	0			
0	1	1	0	1	1	1	1			
0	1	1	1	1	1	1	0			
1	0	0	0	0	0	0	1			
1	0	0	1	0	0	0	1			
1	0	1	0	0	0	0	1			
1	0	1	1	0	0	0	1			
1	1	0	0	0	0	0	1			
1	1	0	1	0	0	0	1			
1	1	1	0	0	1	1	1			
1	1	1	1	0	1	1	1			

$$P = \bar{A}$$

$$Q = B \cdot C$$

$$R = P + Q = \bar{A} + B \cdot C$$

$$S = \overline{P \cdot D} = \overline{\bar{A} \cdot D} = \bar{\bar{A}} + \bar{D} = A + \bar{D}$$

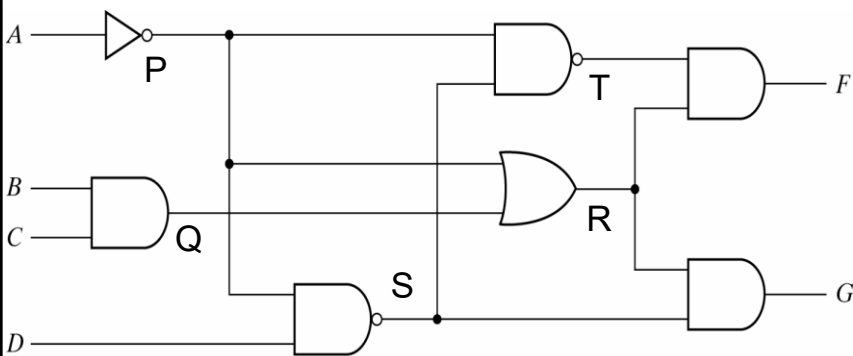

Example 4

A	B	C	D	P	Q	R	S	T	F	G
0	0	0	0	1	0	1	1	0		
0	0	0	1	1	0	1	0	1		
0	0	1	0	1	0	1	1	0		
0	0	1	1	1	0	1	0	1		
0	1	0	0	1	0	1	1	0		
0	1	0	1	1	0	1	0	1		
0	1	1	0	1	1	1	1	0		
0	1	1	1	1	1	1	0	1		
1	0	0	0	0	0	0	1	1		
1	0	0	1	0	0	0	1	1		
1	0	1	1	0	0	0	1	1		
1	1	0	0	0	0	0	1	1		
1	1	0	1	0	0	0	1	1		
1	1	1	0	0	1	1	1	1		
1	1	1	1	0	1	1	1	1		


$$P = \bar{A}$$

$$Q = B \cdot C$$

$$R = P + Q = \bar{A} + B \cdot C$$

$$S = \overline{P \cdot D} = \overline{\bar{A} \cdot D} = \bar{\bar{A}} + \bar{D} = A + \bar{D}$$

$$T = \overline{P \cdot S} = \overline{\bar{A} \cdot (A + \bar{D})} = \overline{\bar{A} \cdot A + \bar{A} \cdot \bar{D}} = \overline{\bar{A} \cdot \bar{D}} = A + D$$

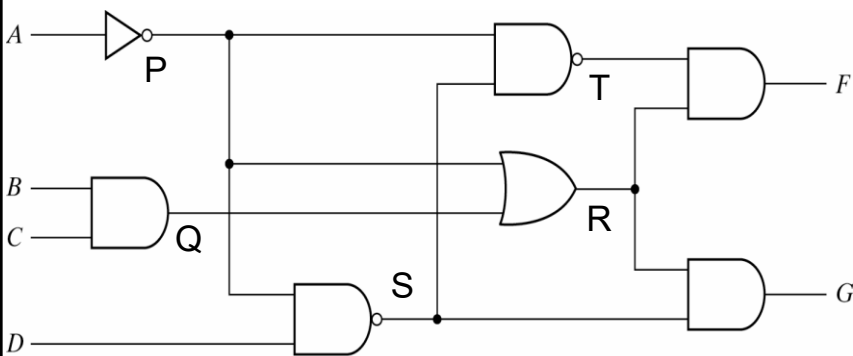

Example 4

A	B	C	D	P	Q	R	S	T	F	G
0	0	0	0	1	0	1	1	0	0	
0	0	0	1	1	0	1	0	1	1	
0	0	1	0	1	0	1	1	0	0	
0	0	1	1	1	0	1	0	1	1	
0	1	0	0	1	0	1	1	0	0	
0	1	0	1	1	0	1	0	1	1	
0	1	1	0	1	1	1	1	0	0	
0	1	1	1	1	1	1	0	1	1	
1	0	0	0	0	0	0	1	1	0	
1	0	0	1	0	0	0	1	1	0	
1	0	1	1	0	0	0	1	1	0	
1	1	0	0	0	0	0	1	1	0	
1	1	0	1	0	0	0	1	1	0	
1	1	1	0	0	1	1	1	1	1	
1	1	1	1	0	1	1	1	1	1	

$$P = \bar{A}$$

$$Q = B \cdot C$$

$$R = P + Q = \bar{A} + B \cdot C$$

$$S = \overline{P \cdot D} = \overline{\bar{A} \cdot D} = \bar{\bar{A}} + \bar{D} = A + \bar{D}$$

$$T = \overline{P \cdot S} = \overline{\bar{A} \cdot (A + \bar{D})} = \overline{\bar{A} \cdot A + \bar{A} \cdot \bar{D}} = \overline{\bar{A} \cdot \bar{D}} = A + D$$

$$F = T \cdot R = (A + D) \cdot (\bar{A} + B \cdot C)$$


$$= A \cdot \bar{A} + A \cdot B \cdot C + \bar{A} \cdot D + B \cdot C \cdot D$$

$$= 0 + A \cdot B \cdot C + \bar{A} \cdot D + (A \cdot B \cdot C \cdot D + \bar{A} \cdot B \cdot C \cdot D)$$

$$= (A \cdot B \cdot C + A \cdot B \cdot C \cdot D) + (\bar{A} \cdot D + \bar{A} \cdot D \cdot B \cdot C)$$

$$= A \cdot B \cdot C \cdot (1 + D) + \bar{A} \cdot D \cdot (1 + B \cdot C)$$

$$= A \cdot B \cdot C + \bar{A} \cdot D$$

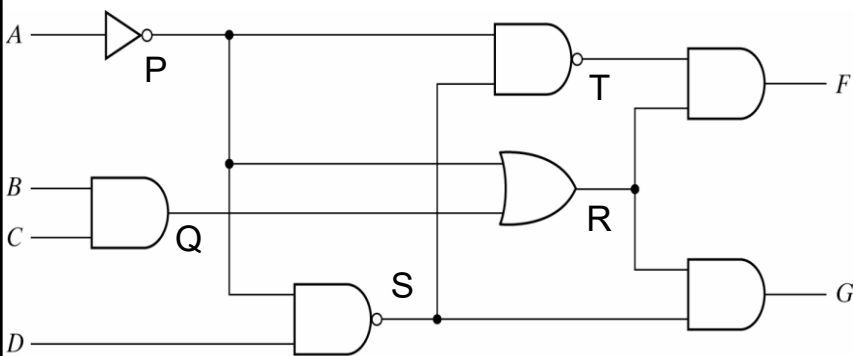

Example 4

A	B	C	D	P	Q	R	S	T	F	G
0	0	0	0	1	0	1	1	0	0	1
0	0	0	1	1	0	1	0	1	1	0
0	0	1	0	1	0	1	1	0	0	1
0	0	1	1	1	0	1	0	1	1	0
0	1	0	0	1	0	1	1	0	0	1
0	1	0	1	1	0	1	0	1	1	0
0	1	1	0	1	1	1	1	0	0	1
0	1	1	1	1	1	1	0	1	1	0
1	0	0	0	0	0	0	1	1	0	0
1	0	0	1	0	0	0	1	1	0	0
1	0	1	1	0	0	0	1	1	0	0
1	1	0	0	0	0	0	1	1	0	0
1	1	0	1	0	0	0	1	1	0	0
1	1	1	0	0	1	1	1	1	1	1
1	1	1	1	0	1	1	1	1	1	1

$$P = \bar{A}$$

$$Q = B \cdot C$$

$$R = P + Q = \bar{A} + B \cdot C$$

$$S = \overline{P \cdot D} = \overline{\bar{A} \cdot D} = \bar{\bar{A}} + \bar{D} = A + \bar{D}$$

$$T = \overline{P \cdot S} = \overline{\bar{A} \cdot (A + \bar{D})} = \overline{\bar{A} \cdot A + \bar{A} \cdot \bar{D}} = \overline{\bar{A} \cdot \bar{D}} = A + D$$

$$F = T \cdot R = (A + D) \cdot (\bar{A} + B \cdot C)$$

$$= A \cdot \bar{A} + A \cdot B \cdot C + \bar{A} \cdot D + B \cdot C \cdot D$$

$$= 0 + A \cdot B \cdot C + \bar{A} \cdot D + (A \cdot B \cdot C \cdot D + \bar{A} \cdot B \cdot C \cdot D)$$

$$= (A \cdot B \cdot C + A \cdot B \cdot C \cdot D) + (\bar{A} \cdot D + \bar{A} \cdot D \cdot B \cdot C)$$

$$= A \cdot B \cdot C \cdot (1 + D) + \bar{A} \cdot D \cdot (1 + B \cdot C)$$

$$= A \cdot B \cdot C + \bar{A} \cdot D$$

$$G = S \cdot R = (A + \bar{D}) \cdot (\bar{A} + B \cdot C)$$

$$= A \cdot \bar{A} + A \cdot B \cdot C + \bar{A} \cdot \bar{D} + B \cdot C \cdot \bar{D}$$

$$= 0 + A \cdot B \cdot C + \bar{A} \cdot \bar{D} + (A \cdot B \cdot C \cdot \bar{D} + \bar{A} \cdot B \cdot C \cdot \bar{D})$$

$$= (A \cdot B \cdot C + A \cdot B \cdot C \cdot \bar{D}) + (\bar{A} \cdot \bar{D} + \bar{A} \cdot \bar{D} \cdot B \cdot C)$$

$$= A \cdot B \cdot C \cdot (1 + \bar{D}) + \bar{A} \cdot \bar{D} \cdot (1 + B \cdot C)$$

$$= A \cdot B \cdot C + \bar{A} \cdot \bar{D}$$

