

CS3350B Computer Organization

Chapter 2: Synchronous Circuits

Part 1: Gates, Switches, and Boolean Algebra

Iqra Batool

Department of Computer Science
University of Western Ontario, Canada

Monday January 29, 2024


Outline

1 Introduction

2 Logic Gates

3 Boolean Algebra

Layers of Abstraction

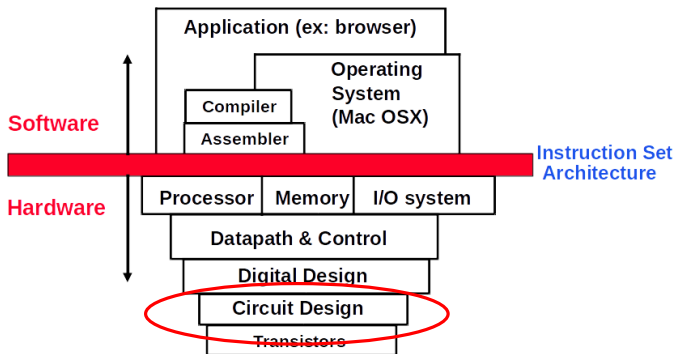

After looking at high-level CPU and Memory we will now go down to the lowest level (that we care about).

Circuit Design vs Digital (Logic) Design

↳ Design of individual circuits vs Using circuits to implement some logic.

Circuit Design

Why do we care?

- Appreciate the limitations of hardware.
- Understand why some things are fast and some things are slow.
- Need circuit design to understand logic design.
- Need logic design to understand **CPU Datapath**.

If you are ever working with:

- Assembly, ISAs,
- Embedded Systems and circuits,
- Specialized computer/logic systems,

you will need circuit and logic design.

Digital Circuits

Everything is **digital**: represented by discrete, individual values.

↳ No gray areas or ambiguity.



Must convert an **analog** – continuously variable – signal to digital.

For us, the analog signal is electricity (voltage).

↳ “High” voltage $\Rightarrow 1$

↳ “Low” voltage $\Rightarrow 0$

Physicality of Circuits

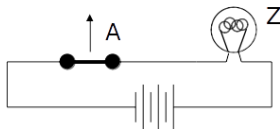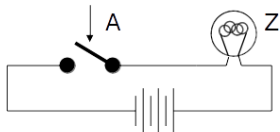

In the end, everything is a switch.

“Input” $\Rightarrow A$

“Output” $\Rightarrow Z$

If A is 0/false then switch is open.

If A is 1/true then switch is closed.


This circuit implements:

$$A \equiv Z$$

Transistors: Electrically Controlled Switches


MOS-FET: Metal-Oxide-Semiconductor Field-Effect Transistor

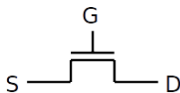- Has a source (S), a drain (D), and a gate (G).
- Applying voltage to G allows current to flow between S and D.
- In reality, transistors, logic gates, SRAM, use CMOS (Complimentary-MOS). But we don't care about transistors really...



n-channel

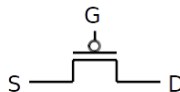opens when voltage at G is low,
closes when voltage at G is high



p-channel

closes when voltage at G is low,
opens when voltage at G is high

Flipping a transistor is *much faster* than moving a physical switch.

↳ Speed of switching a transistor directly related to speed of a CPU

Outline

1 Introduction

2 Logic Gates

3 Boolean Algebra

Logic as Circuits

Propositional Logic: A set of propositions (truth values) combined by some logical connectives.

- Truth values \equiv Binary digital signal
- Logical connectives \equiv **Logic gates**


Logic Gate: A circuit implementing some logical expression/function.

The basics: **AND** (\wedge), **OR** (\vee), **NOT** (\neg).




Arity of a function/gate is the number of inputs.

Gates as Switches

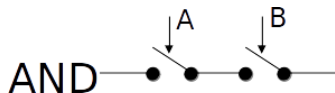

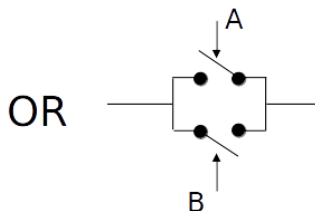- Both A and B must be true/1 to get the circuit to complete.



- Either A or B can be true/1 to get the circuit to complete.

Logic Gates In Detail: AND



$$A \wedge B \equiv C$$

$$A \cdot B \equiv C$$

Truth Table for AND

A	B	$A \wedge B \equiv C$
0	0	0
0	1	0
1	0	0
1	1	1

Logic Gates In Detail: OR




$$A \vee B \equiv C$$

$$A + B \equiv C$$

Truth Table for OR

A	B	$A \vee B \equiv C$
0	0	0
0	1	1
1	0	1
1	1	1

Logic Gates In Detail: NOT

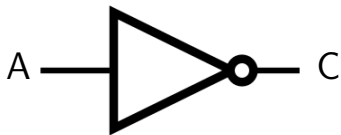

$$\neg A \equiv C$$

$$\overline{A} \equiv C$$

Truth Table for NOT

A	$\neg A \equiv C$
0	1
1	0

More Interesting Logic Gates: NAND



Truth Table for NAND


A	B	$\overline{A \cdot B} \equiv C$
0	0	1
0	1	1
1	0	1
1	1	0

$$\neg(A \wedge B) \equiv C$$

$$\overline{A \cdot B} \equiv C$$

$$A \mid B$$

More Interesting Logic Gates: NOR

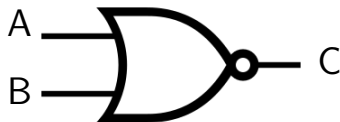

$$\neg(A \vee B) \equiv C$$

$$\overline{A + B} \equiv C$$

Truth Table for NOR

A	B	$\overline{A + B} \equiv C$
0	0	1
0	1	0
1	0	0
1	1	0

More Interesting Logic Gates: XOR (Exclusive OR)



$$A \oplus B \equiv C$$

Truth Table for XOR

A	B	$A \oplus B \equiv C$
0	0	0
0	1	1
1	0	1
1	1	0

Outline

1 Introduction

2 Logic Gates

3 Boolean Algebra

The Algebra of Logic Gates

Due to the equivalence of truth values and binary digital signals, **Boolean Algebra** is heavily used discussing circuitry.

Associativity:

$$(A + B) + C \equiv A + (B + C)$$

$$(A \cdot B) \cdot C \equiv A \cdot (B \cdot C)$$

Commutativity:

$$A + B \equiv B + A$$

$$A \cdot B \equiv B \cdot A$$

Distributivity:

$$A + (B \cdot C) \equiv (A + B) \cdot (A + C)$$

$$A \cdot (B + C) \equiv (A \cdot B) + (A \cdot C)$$

Identity:

$$A + 0 \equiv A$$

$$A \cdot 1 \equiv A$$

Annihilation:

$$A + 1 \equiv 1$$

$$A \cdot 0 \equiv 0$$

Idempotence:

$$A + A \equiv A$$

$$A \cdot A \equiv A$$

Boolean Algebra: More Interesting Laws

Absorption:

$$A \cdot (A + B) \equiv A$$

$$A + (A \cdot B) \equiv A$$

Double Negation

$$\overline{\overline{A}} \equiv A$$

Complementation:

$$A + \overline{A} \equiv 1$$

$$A \cdot \overline{A} \equiv 0$$

De Morgan's Laws:

$$\overline{A + B} \equiv \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} \equiv \overline{A} + \overline{B}$$

Look familiar?

↳ Definitions of NOR and NAND.

Proving De Morgan's Laws

Proof by Exhaustion:

- ↳ The easiest way to prove something is to write out each expression's truth table.

$$\overline{A + B} \equiv \overline{A} \cdot \overline{B}$$

A	B	$A + B$	$\overline{A + B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

A	B	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

Simplifying Expressions with Boolean Algebra (1/2)

$$\overline{xyz} + \overline{xy}z$$

$$\overline{xyz} + \overline{xy}z \equiv \overline{xy}(\overline{z} + z) \quad \text{Factor } \overline{xy}$$

$$\equiv \overline{xy}(1) \quad \text{Complementation of } z$$

$$\equiv \overline{xy} \quad \text{Identity with } \overline{xy}$$

x	y	z	\overline{xyz}	$\overline{xy}z$	$\overline{xyz} + \overline{xy}z$
0	0	0	1	0	1
0	0	1	0	1	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	0	0

Note: $\overline{AB} \implies \overline{A} \cdot \overline{B}$; otherwise use $\overline{A \cdot B}$ or $\overline{(AB)}$ for $A \mid B$.

Simplifying Expressions with Boolean Algebra (2/2)

Sometimes a truth table is too challenging...

↳ For v variables a truth table has 2^v rows.


$$\overline{(\overline{x} + \overline{z})} (abcd + xz) \implies 6 \text{ variables, } 64 \text{ rows}$$

Instead we can simplify using the laws of Boolean algebra:

$$\begin{aligned} \overline{(\overline{x} + \overline{z})} (abcd + xz) &\equiv \overline{\overline{xz}} (abcd + xz) && \text{De Morgan's Law} \\ &\equiv xz (abcd + xz) && \text{Double negation of } x \text{ and } z \\ &\equiv xz && \text{Absorption} \end{aligned}$$

Simplifying Expressions for Simplified Circuits

$$y = ((ab) + a) + c$$

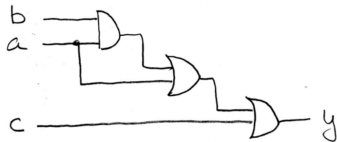

$$y \equiv (ab + a) + c$$

$$\equiv a(b + 1) + c \quad \text{Factor } a$$

$$\equiv a(1) + c \quad \text{Annihilation}$$

$$\equiv a + c \quad \text{Identity}$$



Canonical Forms

Different standard or **canonical forms**.

- **Conjunctive Normal Form** (CNF) \Rightarrow AND of ORs
↳ "Product-of-sums"
- **Disjunctive Normal Form** (DNF) \Rightarrow ORs of ANDs
↳ "Sum-of-products"

$$\text{CNF} \quad (a + b) \cdot (\bar{a} + b) \cdot (\bar{a} + \bar{b})$$

$$\text{DNF} \quad ab + \bar{a}b + \bar{a}\bar{b}$$

- Every variable should appear in every sub-expression.
↳ Products for DNF, Sums for CNF.
↳ Some authors call this "Full DNF" or "Full CNF".
- Every boolean expression can be converted to a canonical form.
- DNF more useful and practical \Rightarrow truth tables.

Truth Tables and Disjunctive Normal Forms

We can get a DNF expression directly from a truth table.

- a, b, c are inputs, f is output.
- Create one product term for every entry in the table with $f \equiv 1$.
- Put \bar{x} in product if x is false in that row.
- Put x in product if x is true in that row.
- OR all products together.

a	b	c	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$\implies \overline{abc} + \overline{ab}\bar{c} + \overline{a}b\bar{c} + abc$$

Functional Completeness

Functional Completeness - A set of functions (operators) which can adequately describe every operation and outcome in an algebra.

- For Boolean algebra the classical set of operators: $\{+, \cdot, \neg\}$ is functionally complete but not **minimal**.
- Thanks to De Morgan's Law we only need one of AND or OR.
- The sets $\{+, \neg\}$ and $\{\cdot, \neg\}$ are both functionally complete and minimal.
 - ↳ **minimal** - removing any one of the operators would make the set functionally *incomplete*.
- NAND alone is functionally complete; so is NOR alone.

NAND is Functionally Complete

NAND alone is functionally complete.

- $\text{NAND} \equiv |$
- To prove functional completeness simply show that the operators of the set can mimic the functionality of the set $\{+, \cdot, \neg\}$.

$$\neg X \equiv X | X$$

$$X \cdot Y \equiv \overline{X|Y} \equiv (X|Y) | (X|Y)$$

$$X + Y \equiv \overline{\overline{X+Y}} \equiv \overline{\overline{X} \cdot \overline{Y}} \equiv (X|X) | (Y|Y)$$

X	\overline{X}	$X \cdot X$	$\overline{X \cdot X}$
0	1	0	1
1	0	1	0

X	Y	$A \equiv X Y$	$A A$
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

X	Y	\overline{X}	\overline{Y}	$\overline{X Y}$
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1

Summary

Boolean algebra can simplify circuits.

- Remove variables that the output does not depend on.
- Simplifies expression, removing needless gates.
- Space and time complexity improved!

Truth tables, canonical forms, functional completeness.

Help generating truth tables:

- <https://web.stanford.edu/class/cs103/tools/truth-table-tool/>